

Physics 111A Lab 5

Pre-Lab Questions

- 1) To increase gain, either R_s can decrease or R_D can increase. Arbitrarily increasing R_D values would cause the current to decrease, making it harder to read the signal. Decreasing R_s would cause r_s to become dominant and make the gate fall out of the ideal regime.
- 2) A 100 MHz carrier modulated at 5 kHz extends between a band of frequencies from 99.995 - 100.005 MHz.
- 3) One gate is held at a constant V_{GS} being connected to ground while the other is able to be modified. This means that if by changing the V_{GS} of one gate, you change how much current can pass through its side of the circuit and in turn how much has to go through the other gate. This then means that a higher current through the grounded gate means a lower V_{DS} since the V_{DS} across R_D will increase.

Lab Exercises:

Problem R5.1:

$$V_{GS} = 0.1 \text{ mV}$$

$$V_{foll} = 1.317 \text{ V}$$

$$V_{out} = 7.97 \text{ V}$$

$$I_{DS} = 3.95 \text{ mA}$$

$$V_{DS} = 6.65 \text{ V}$$

a) $\frac{V_{foll}}{V_{in}} = G = 0.757$

$$G = \frac{R_s}{R_s + r_s} \Rightarrow G(R_s + r_s) = R_s \Rightarrow r_s = \left(\frac{1-G}{G}\right) R_s = 106 \Omega$$

b) $V_{out} = 163 \text{ mV}$

$$G = -2.329$$

$$\text{exact } G = -\frac{R_D}{R_s + r_s} = -\frac{1k\Omega}{330 + 106} = -2.29$$

$$\text{approx } G \approx -\frac{R_D}{R_s} = -3.03$$

The approximate gain equation can be seen as close enough.

V_{out} is inverted

$$\langle V_{out} \rangle = 7.96 \text{ V}$$

c) max amp $V_{out} = 4.14 \text{ V}$



The amplitude is limited by V_{out} being unable to exceed 12V, the V_o

Problem R5.2

$R_D (\text{k}\Omega)$	G	$\langle V_{out} \rangle (\text{V})$
1	-2.329	7.96
1.5	-3.44	5.97
2.2	-4.44	3.34
3	-1.02	1.64
5.1	-0.124	0.87
7.5	-0.071	0.58
10	-0.054	0.44

The largest gain was -4.44.

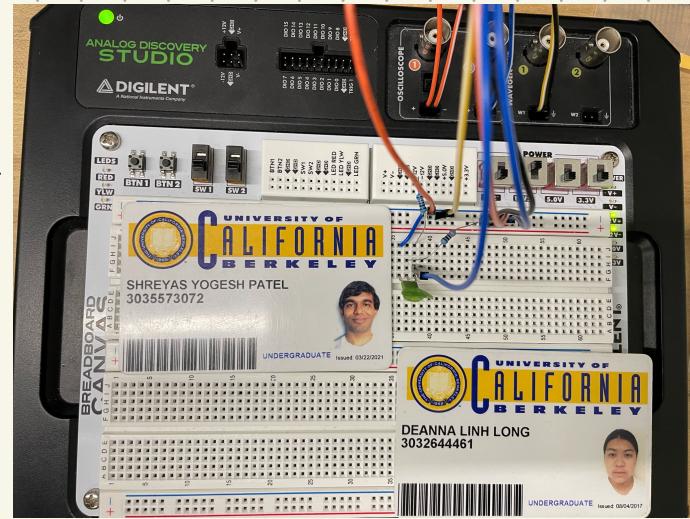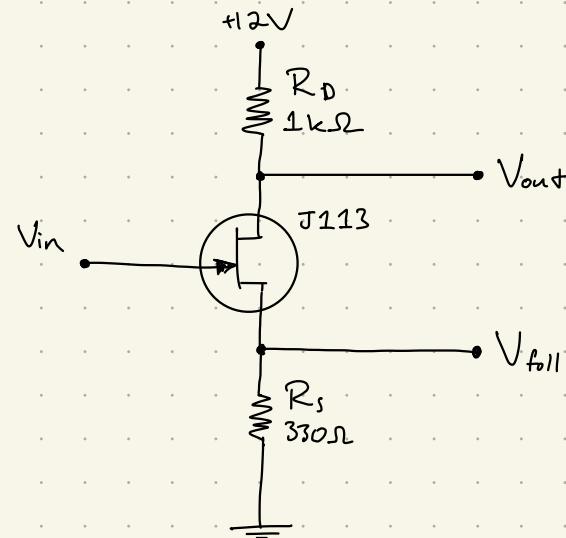The gain peaks when $\langle V_{out} \rangle \approx \text{max } V_{out}$ amplitude and decreases when R_D changes this value to lower or higher values.



Problem RS.3

$R_s (\Omega)$	G	$-\frac{R_o}{R_s}$	$r_s (\Omega)$
100	-4.64	-10	115.5
47	-1.256	-21.27	749.2
22	-0.65	-45.45	1516.5
10	-0.509	-100	1954.6
0	-0.453	∞	2207.5

The gain is smaller and smaller as R_s decreases while the simplified gain formula increases.

$$G_2 = -\frac{R_o}{R_s + r_s} \Rightarrow r_s = -\frac{R_o + G_2 R_s}{G_2}$$

Problem RS.4


$$G_2 = \frac{R_o}{R_s}, Z_s = \left(\frac{1}{R} + j\omega C \right)^{-1} = \left(\frac{1+j\omega RC}{R} \right)^{-1} = \frac{R}{1+j\omega RC} = \frac{R(1-j\omega RC)}{1+(\omega RC)^2}, R_s = \frac{R}{1+(\omega RC)^2}, G_2 = \frac{G_0}{\sqrt{2}}$$

$$\log G_2 = 3 \Rightarrow \log \left(\frac{R_o(1+\omega RC)^2}{R} \right) = 3 \Rightarrow \frac{R_o}{R} (1+\omega RC)^2 = 10^3 \Rightarrow 1 + (\omega RC)^2 = \frac{10^3 R}{R_o} \Rightarrow \omega RC = \left(\frac{10^3 R}{R_o} - 1 \right)^{\frac{1}{2}} \Rightarrow \omega = \frac{1}{RC} \left(\frac{10^3 R}{R_o} - 1 \right)^{\frac{1}{2}}$$

$$G = \frac{1}{\sqrt{2}} G_0 \Rightarrow$$



JFET	$G @ \omega = 200 \text{ kHz}$	$R_s = 830\Omega$
0	19.5 dB	
1	19.6 dB	
2	19.5 dB	
3	19.3 dB	
9	19.4 dB	
Ave.	19.45 dB	
STD	0.123	

JFET	$G @ \omega = 200 \text{ kHz}$	$R_s = 0\Omega$
0	-7.01 dB	
1	-5.34 dB	
2	-7.96 dB	
3	-5.625 dB	
9	-8.4 dB	
Ave.	-6.88	
STD	1.348	

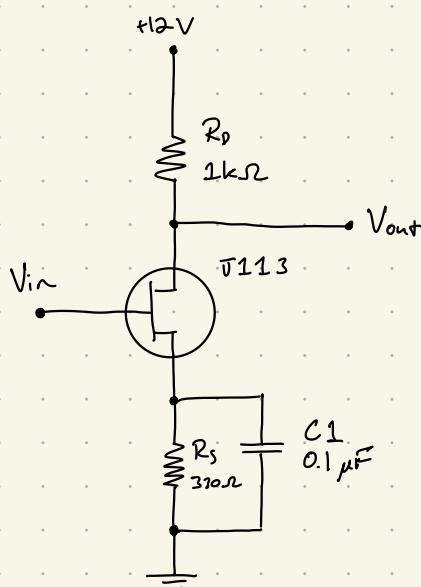


Problem R 5.5

c)

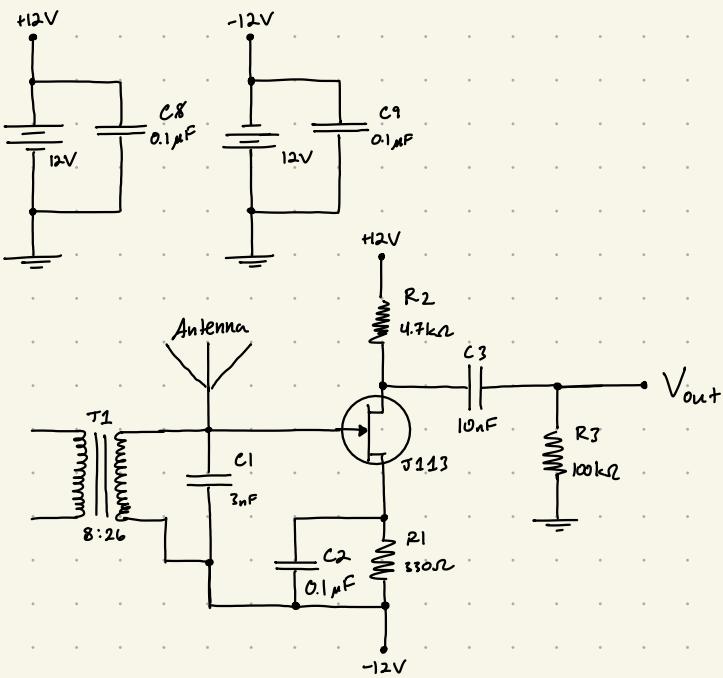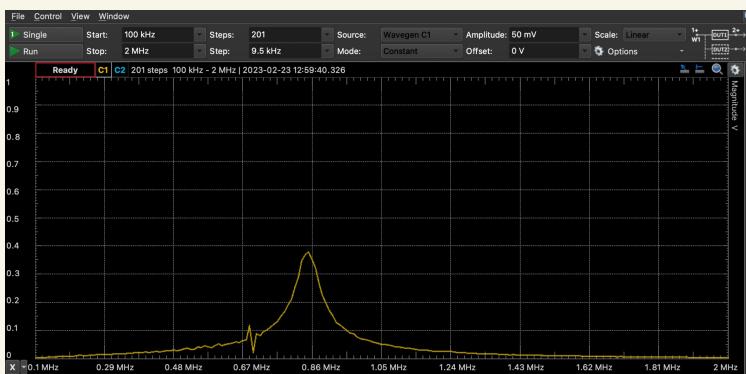

d)

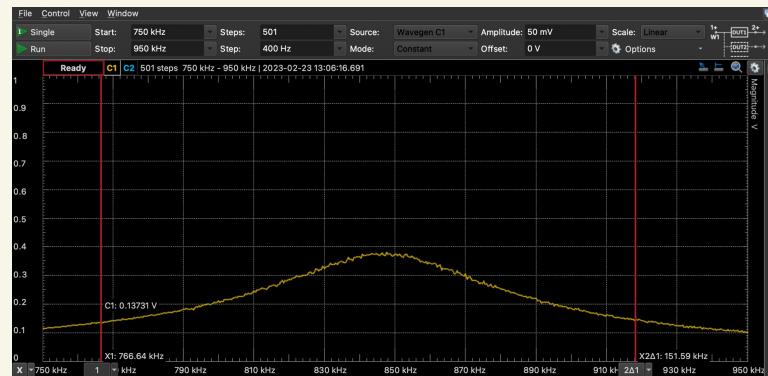

$$f_0 = 847.73 \text{ kHz}$$

$$2\pi f_0 = \frac{1}{\sqrt{LC}} \Rightarrow L = \frac{1}{(2\pi f_0)^2 C} = \frac{1}{(2\pi(847.73 \text{ kHz}))^2 (3 \text{ nF})} = 11.75 \mu\text{H}$$

The number of coils and how tightly they were wound as well as the antenna placement and length are all possible sources of error.

$$V_{\text{peak}} = 0.37895 \text{ V}$$

$$V_{-3\text{dB}} = 816.73 \text{ kHz}, 876.2 \text{ kHz}$$

$$\text{e) } Q = \frac{847.73 \text{ kHz}}{(876.2 - 816.73) \text{ kHz}} = 14.25$$

$$\text{i) } Q = R_{\text{par}} \sqrt{\frac{C}{L}} \Rightarrow R_{\text{par}} = Q \sqrt{\frac{L}{C}} = 14.25 \sqrt{\frac{11.75 \mu\text{H}}{3 \text{ nF}}} = 891.812 \Omega$$

It is not plausible that R_{par} is the cause of the low Q since the only R_{par} is R_g of the JFET which is much higher than the calculated R_{par} .

$$\text{ii) } Q = \frac{1}{R_{\text{ser}}} \sqrt{\frac{L}{C}} \Rightarrow R_{\text{ser}} = \frac{1}{Q} \sqrt{\frac{L}{C}} = \frac{1}{14.25} \sqrt{\frac{11.75 \mu\text{H}}{3 \text{ nF}}} = 4.392 \Omega$$

for 22 gauge, $\frac{R}{l} = 52.9392 \Omega \text{ km}^{-1}$, $l \approx 3 \text{ m}$, $R_{\text{wire}} = 0.1588 \Omega$
resistance of the wire is too low to explain the low Q

Our BW is 59.47 kHz, so up to ~6 stations can be received simultaneously.

$$f) \text{ predicted } f_0 = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{(11.75\mu H)(1nF)}} = 1.47 \text{ MHz}$$

$$\text{measured } f_0 = 1.33 \text{ MHz}$$

The resonant frequency does change. Measured value has a % diff of 9.5% from predicted.

$$g) \text{ peak } V_{out} = 0.39109 \text{ V}$$

$$\text{peak } V_{ci} = 0.02783 \text{ V}$$



$$G = 14.05$$

$$h) \omega = \frac{1}{\sqrt{LC}} \Rightarrow C = \frac{1}{\omega^2 L} = \frac{1}{(2\pi f)^2 L}$$


$$f = 740 \text{ kHz}, C = \frac{1}{(2\pi(740 \text{ kHz}))^2 (11.75 \mu H)} = 3.94 \times 10^{-9} F = 3.94 \text{ nF} \approx 4 \text{ nF}$$




Problem R 5.6

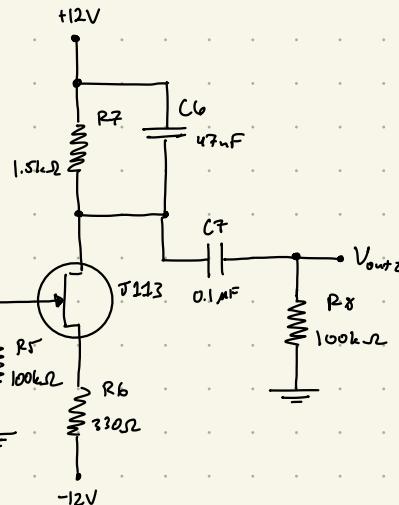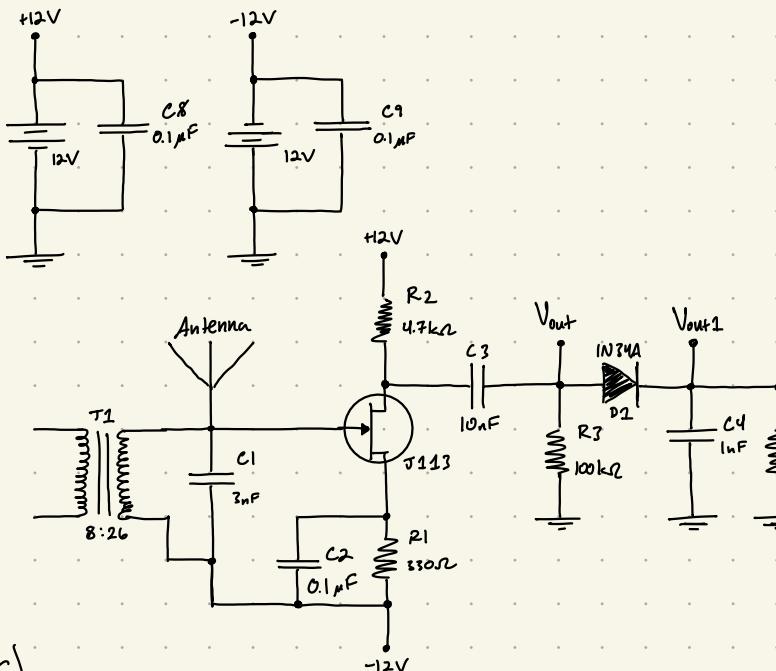


c)

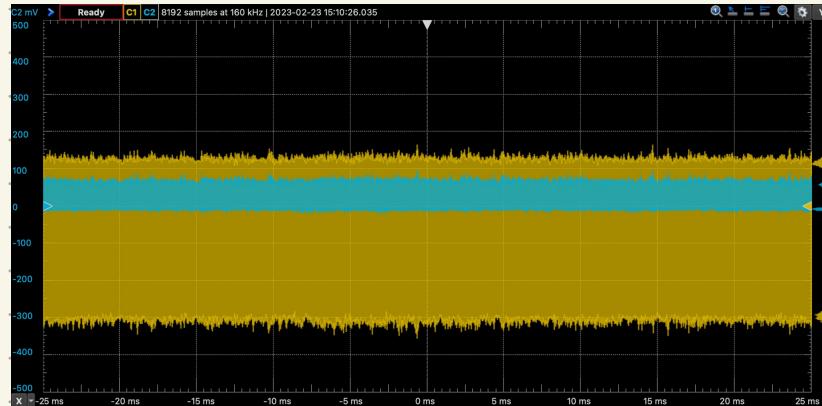


d)

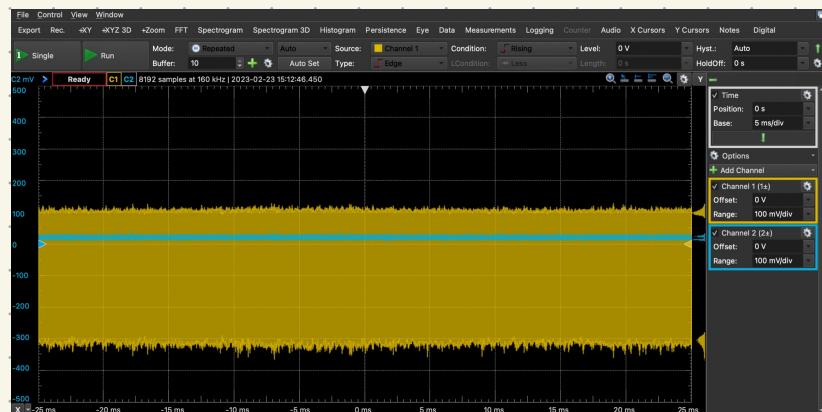

e)

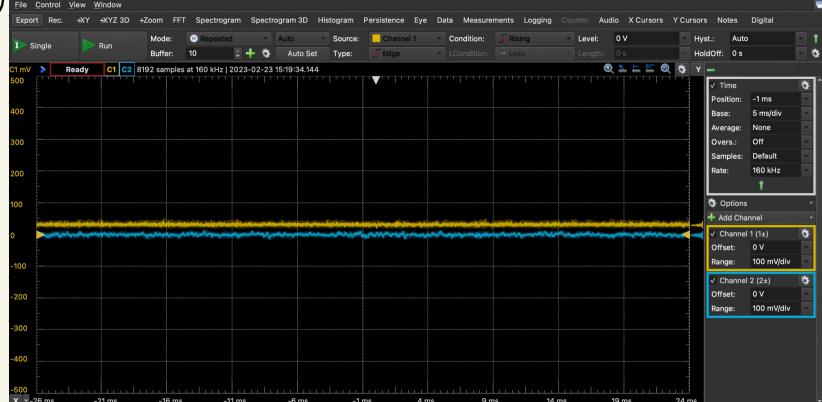


Problem RS.7

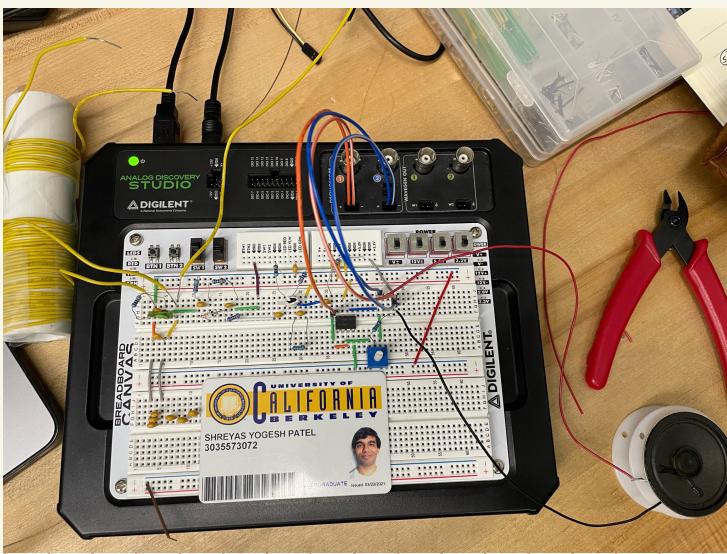


d) station	frequency (kHz)	C_1 (nF)	$C_1 = \frac{1}{(2\pi f)^2 L}$
KCBS	740	3.94	
KVTO	1400	1.1	
KMKY	1310	1.26	

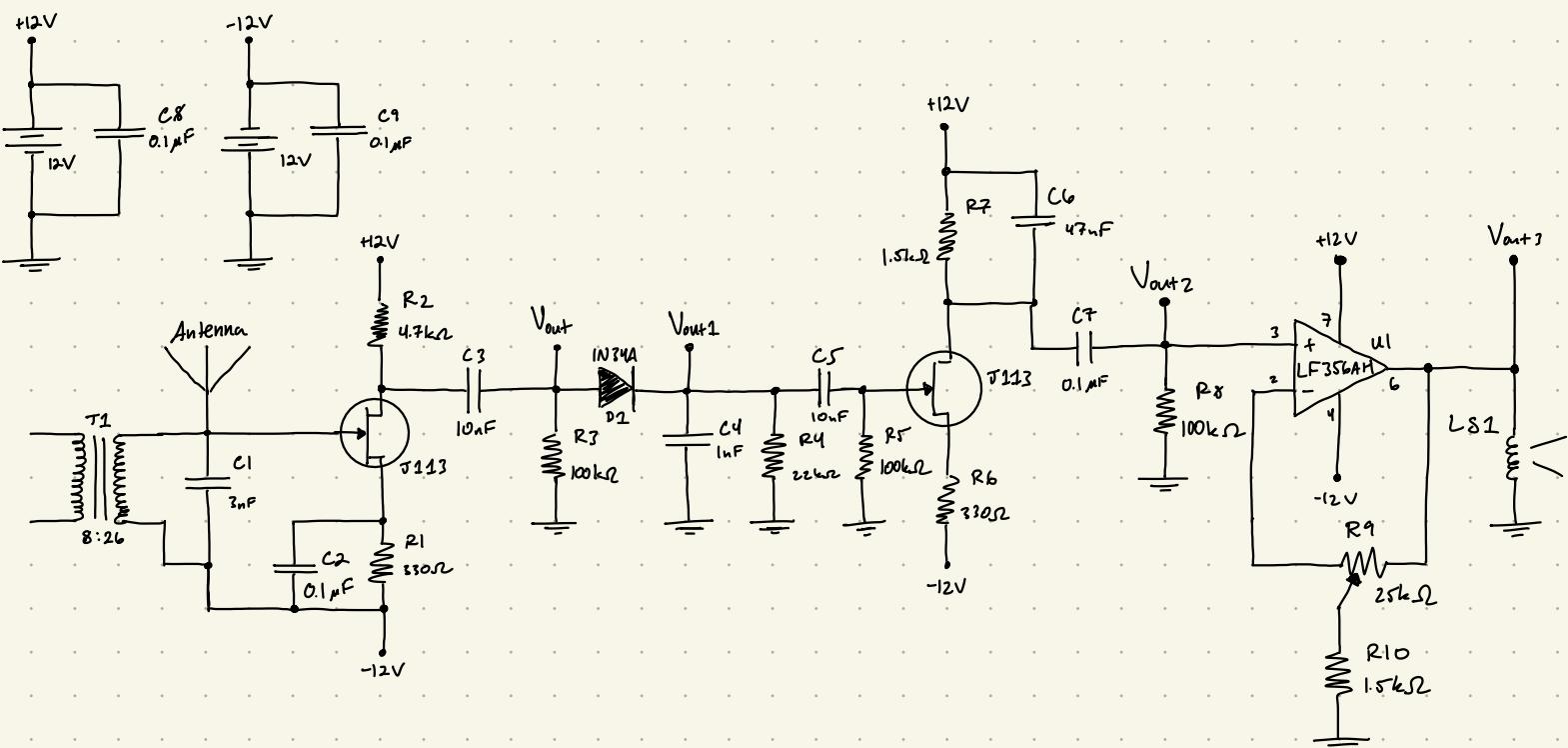We used a fake radio source using waveforms.




Problem R5.8

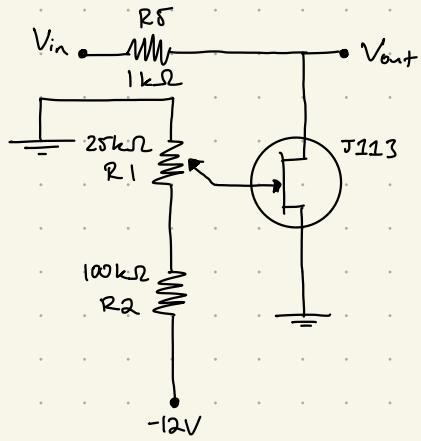


The higher V_{out} gets, the more distorted V_{out} becomes, becoming more distorted and non-linear.

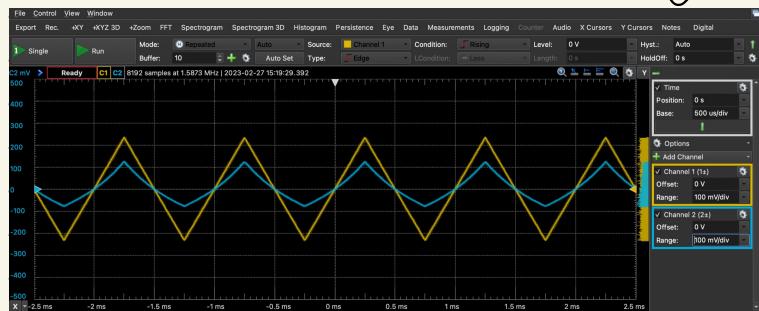
The largest signal to pass relatively undistorted is $V_{in} = 240\text{mV}$.



Problem R5.9

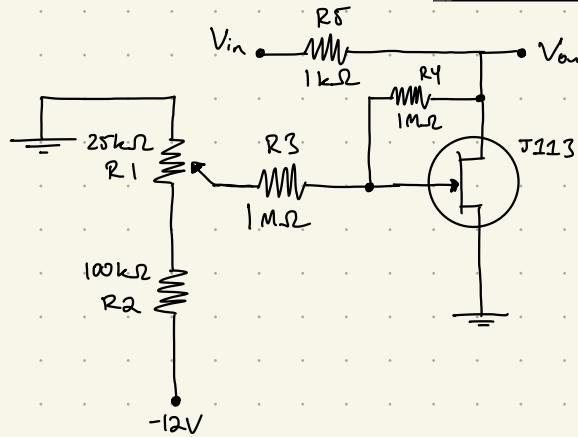



Largest is now $V_{in} = 400\text{mV}$.

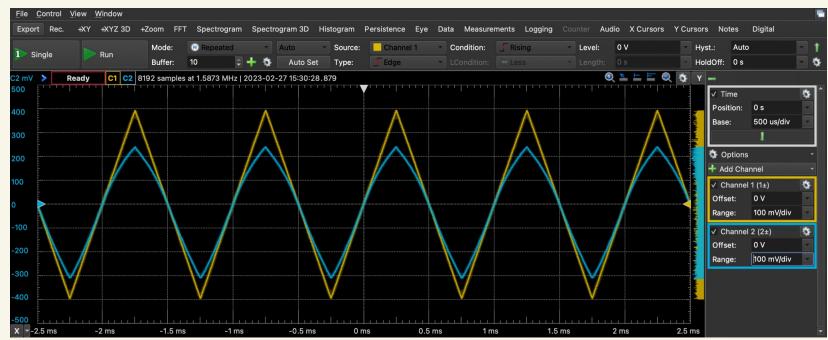

$$\text{Attenuation: } \frac{V_{out}}{V_{in}} = \frac{391.1\text{mV}}{238.6\text{mV}} = 0.61$$

$$V_{out} = \frac{R_{DS}}{R_{DS} + R_S} V_{in} \Rightarrow A = \frac{R_{DS}}{R_{DS} + R_S} \Rightarrow A R_{DS} + A R_S = R_{DS} \Rightarrow R_{DS} = \frac{A}{1-A} R_S = \frac{0.61}{0.39} (1\text{k}\Omega) = 1.564\text{k}\Omega$$

Problem RS.10

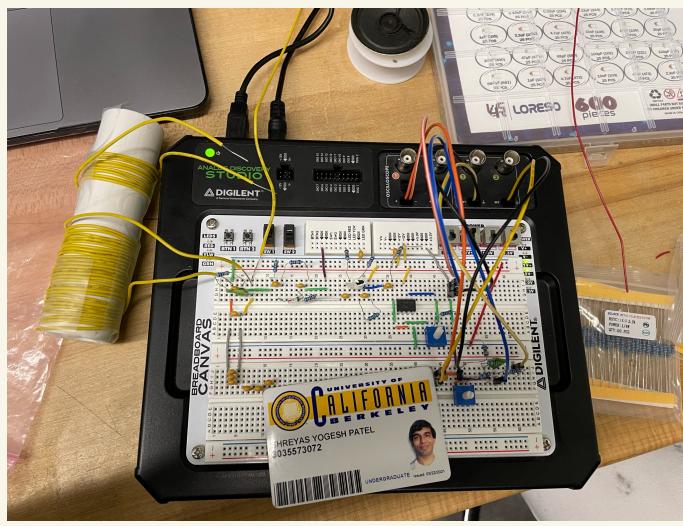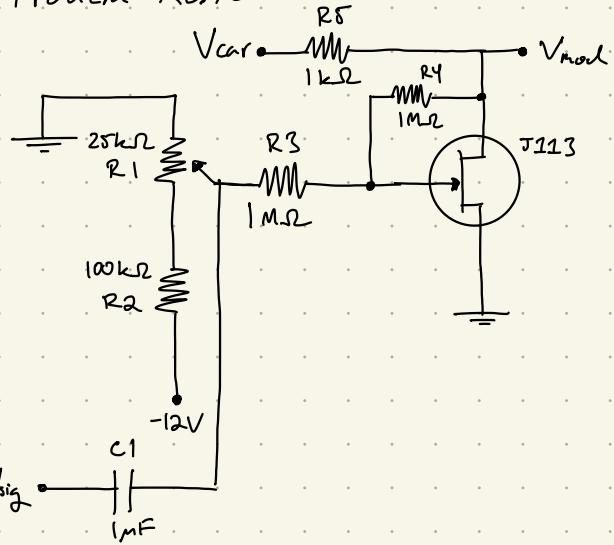


Problem RS.11

$$f = 490 \text{ kHz}, C_1 = \frac{1}{(2\pi f)^2 L} = 8.978 \text{ nF} \approx 9 \text{ nF}$$

used $C_1 = 8.7 \text{ nF}$, 4 nF capacitors in parallel with 4.7 nF capacitor
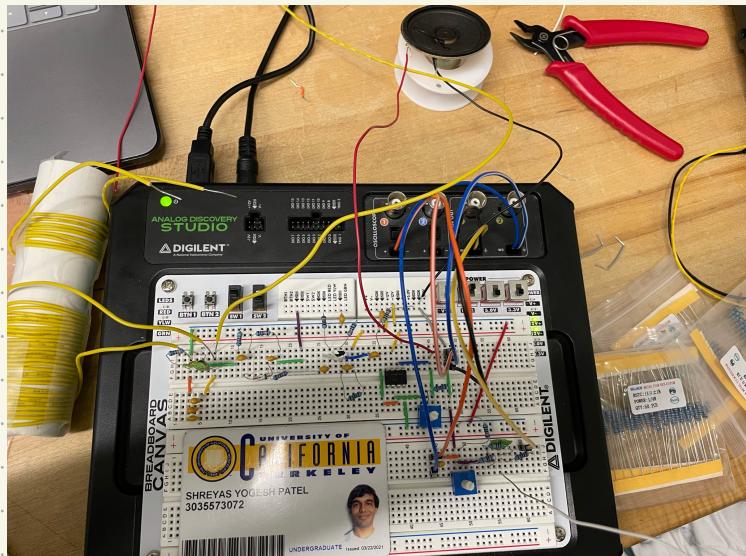
$$f = 400 \text{ kHz}, C_1 = 13.47 \text{ nF} \approx 13.5 \text{ nF}$$



Problem R.S.12

a) $V_+ = 95.93 \text{ mV}$, $V_- = -101.25 \text{ mV} \Rightarrow V_d = \frac{1}{2}(95.93 + 101.25) = 98.59 \text{ mV}$

$$V_{\text{out}} = 0.8 \text{ V}, V_{\text{ideal}} = \frac{1}{2}(100 + 100) = 100 \text{ mV}$$

$$G_d = \frac{0.8 \text{ V}}{98.59 \text{ mV}} = 8.11, \text{ ideal } G_d = \frac{0.8 \text{ V}}{100 \text{ mV}} = 8$$

b) V_{out} is in phase with V_+ so its phase is also 0° .

c) $V_+ = 99.78 \text{ mV}$, $V_{\text{out}} = 0.35 \text{ V}$, $V_- = 0 \text{ V}$


$$V_d = \frac{1}{2}(99.78 - 0) = 49.89 \text{ mV}$$

$$\frac{V_{\text{out}}}{\sqrt{V_d^2 + V_+^2}} = 3.14, V_{\text{out}} \text{ is in phase with } V_+ \text{ still}$$

$$V_c = \frac{1}{2}(99.78 + 0) = 49.89 \text{ mV}$$

d) $V_+ = 0 \text{ V}$, $V_{\text{out}} = 0.36 \text{ V}$, $V_- = -100.8 \text{ mV} \Rightarrow V_d = \frac{1}{2}(100.8) = 50.4 \text{ mV} \Rightarrow G_d = \frac{V_{\text{out}}}{V_d} = 7.14$
 V_{out} is 180° out of phase with V_-

e) $V_+ = 99.89 \text{ mV}$, $V_{\text{out}} = -0.121 \text{ V}$, $V_- = 98.9 \text{ mV} \Rightarrow V_d = 0.495 \text{ mV}$, $V_c = 99.395 \text{ mV} \Rightarrow G_d = \frac{V_{\text{out}}}{V_c} = -1.22$
 $G_c = \frac{R_o}{2R_1 + R_s} = \frac{3 \text{ k}\Omega}{2(10 \text{ k}\Omega) + 100 \text{ }\Omega} = 0.149$, The gain is an order magnitude off.

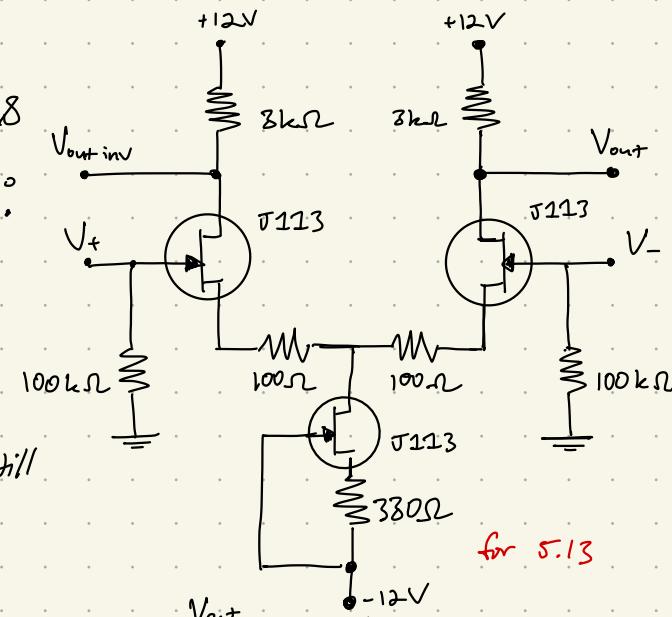

for 5.13

Problem R.S.13

a) $V_+ = 99.15 \text{ mV}$, $V_- = -100.76 \text{ mV}$

$$V_{\text{out}} = 1.1619 \text{ V}$$

$$V_d = \frac{1}{2}(V_+ - V_-) = \frac{1}{2}(99.15 + 100.76) = 99.955 \text{ mV}$$

$$V_c = \frac{1}{2}(V_+ + V_-) = \frac{1}{2}(99.15 - 100.76) = -0.805 \text{ mV}$$

$$G_d = \frac{V_{\text{out}}}{V_d} = \frac{1.1619 \text{ V}}{99.955 \text{ mV}} = 11.6$$

$$G_c = \frac{V_{\text{out}}}{V_c} = \frac{1.1619 \text{ V}}{-0.805 \text{ mV}} = -1441$$



The performance improves because the current source is self-biased and more strictly regulates the current flow through the differential amplifier.

b) We warmed the JFET with an input of V_+ and it decreased V_{outinv} , creating an offset between V_{out} and V_{outinv} .

When both JFETs are warmed simultaneously, there is no change.

c) JFETs that are unmatched causes a difference between V_{out} and V_{outinv} in order of magnitude of several volts.