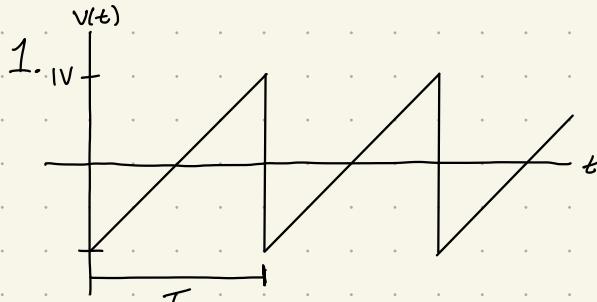


Physics IIIA Lab 2

Pre-Lab Questions:



$$\text{for } 0 \leq t \leq T : V(t) = \frac{2}{T}t - 1$$

$$b_0 = \frac{1}{T} \int_0^T \frac{2}{T}t - 1 dt = \frac{1}{T} \left[\frac{1}{T}t^2 - t \right]_0^T = \left[\left(1 - \frac{1}{T}\right) - \left(-\frac{1}{T}\right) \right] = 0$$

$$b_n = \frac{2}{T} \int_0^T \left(\frac{2}{T}t - 1 \right) \cos \left(\frac{2\pi n t}{T} \right) dt = \frac{2}{T} \int_0^T \frac{2}{T}t \cos \left(\frac{2\pi n t}{T} \right) dt - \int_0^T \cos \left(\frac{2\pi n t}{T} \right) dt$$

$$= \frac{2}{T} \left[\int_0^T \frac{2}{T}t \cos \left(\frac{2\pi n t}{T} \right) dt - \int_0^T \cos \left(\frac{2\pi n t}{T} \right) dt \right]$$

$$a_n = \frac{2}{T} \int_0^T \left(\frac{2}{T}t - 1 \right) \sin \left(\frac{2\pi n t}{T} \right) dt$$

$$= \frac{2}{T} \left[\frac{2}{T} \int_0^T t \sin \left(\frac{2\pi n t}{T} \right) dt - \int_0^T \sin \left(\frac{2\pi n t}{T} \right) dt \right]$$

$$= \frac{2}{T} \left\{ \frac{2}{T} \left[-\frac{1}{2\pi n} t \cos \left(\frac{2\pi n t}{T} \right) \right]_0^T + \frac{1}{\pi n} \int_0^T \cos \left(\frac{2\pi n t}{T} \right) dt \right\}$$

$$= \frac{2}{T} \left\{ -\frac{1}{\pi n} \left[T \cos \left(2\pi n \right) \right] + \frac{T}{2\pi^2 n^2} \left[\sin \left(\frac{2\pi n t}{T} \right) \right]_0^T \right\}$$


$$= \frac{2}{T} \left(-\frac{1}{\pi n} \right) = -\frac{2}{\pi n}$$

$$= \frac{2}{T} \left\{ \left[\frac{2}{T} \frac{1}{2\pi n} t \sin \left(\frac{2\pi n t}{T} \right) \right]_0^T - \frac{1}{\pi n} \int_0^T \sin \left(\frac{2\pi n t}{T} \right) dt - \left[\frac{T}{2\pi n} \sin \left(\frac{2\pi n t}{T} \right) \right]_0^T \right\}$$

$$= \frac{2}{T} \left\{ \frac{1}{\pi n} \left[T \sin \left(2\pi n \right) - 0 \right] - \frac{1}{\pi n} \left[-\frac{T}{2\pi n} \cos \left(\frac{2\pi n t}{T} \right) \right]_0^T \right\}$$

$$= \frac{2}{T} \frac{T}{2\pi^2 n^2} (\cos(2\pi n) - 1) = \frac{1}{\pi^2 n^2} (1 - 1) = 0$$
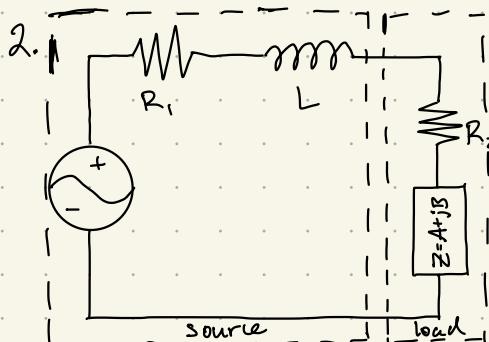
$$\underline{b_0 = 0, b_n = 0, a_n = -\frac{2}{\pi n}}$$



$$a) Z_L = \frac{V(t)}{I(t)} = j\omega L, \quad L = \frac{\mu_0 K N^2 A}{c}, \quad \mu_0 \text{ permeability of core}$$

$$H(\omega) = \frac{1 - j\omega \frac{L}{R}}{1 + (\omega \frac{L}{R})^2}, \quad G(\omega) = \frac{1}{\sqrt{1 + (\omega \frac{L}{R})^2}}, \quad \phi(\omega) = -\tan^{-1}(\omega \frac{L}{R})$$

$$Z_{\text{tot}} = Z_{R_1} + Z_L + Z_{R_2} + Z = R_1 + j\omega L + R_2 + Z$$

$$P_L = I_{\text{rms}}^2 R_L = \frac{1}{2} \left(\frac{V_s}{|Z_{\text{tot}}|} \right)^2 R_L$$

P_L is maximized when $Z_{\text{source}} = Z_{\text{load}}^*$ and the complex parts cancel

$$Z_{\text{source}} = Z_{R_1} + Z_L = R_1 + j\omega L, \quad Z_{\text{load}}^* = Z_{R_2}^* + Z^* = R_2 + A - jB$$

$$R_1 + j\omega L = R_2 + Z^* \Rightarrow Z^* = R_1 - R_2 + j\omega L \Rightarrow Z = R_1 - R_2 - j\omega L$$

$$R_1 + j\omega L = R_2 + A - jB \Rightarrow R_1 = R_2 + A \Rightarrow A = R_1 - R_2$$


$$\omega L = -B \Rightarrow B = -\omega L$$

$$Z = R_1 - R_2 - j\omega L$$

$$R = R_1 - R_2, \quad \frac{1}{j\omega C} = -j\omega L \Rightarrow -\frac{j}{\omega C} = -j\omega L$$

$$\Rightarrow \frac{1}{\omega C} = \omega L \Rightarrow C = \frac{1}{\omega^2 L}$$

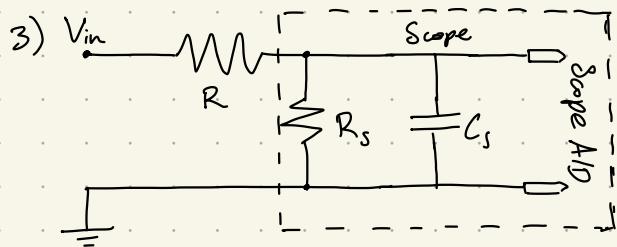You would insert a resistor with $R = R_1 - R_2$ and capacitor with $C = \frac{1}{\omega^2 L}$ in series.



$$R_s = 1 \text{ M}\Omega$$

$$b) R = R_s, G(\omega) = \frac{R_s}{\sqrt{4R_s^2 + \omega^2 C_s^2 R_s^2}}$$

$$\frac{R_s}{R_s \sqrt{4 + \omega^2 C_s^2 R_s^2}} = \frac{1}{2\sqrt{2}} \Rightarrow \frac{1}{\sqrt{4 + \omega^2 C_s^2 R_s^2}} = \frac{1}{2\sqrt{2}} \Rightarrow 4 + \omega^2 C_s^2 R_s^2 = 8 \Rightarrow \omega^2 = \frac{4}{C_s^2 R_s^2} \Rightarrow \omega = \frac{2}{R_s C_s}$$

4) $k=1, N_{12} = \frac{N_1}{N_2}, L_1$ drives load $Z_L = R$

$$Z_{in} = Z_L \left(1 + \frac{j\omega L_2 (1-k^2)}{Z_L} \right) \cdot \left(N_{21}^2 \left(1 + \frac{Z_L}{j\omega L_2} \right) \right)^{-1} = R \left(1 + \frac{j\omega L_2 (1-k^2)}{R} \right) \cdot \left(\frac{N_2^2}{N_1^2} \left(1 + \frac{R}{j\omega L_2} \right) \right)^{-1}$$

$$\frac{N_1}{N_2} = \sqrt{\frac{L_1}{L_2}} = N_{12} \Rightarrow L_2 = \frac{L_1}{N_{12}^2}$$

$$= R \cdot \left(\frac{N_2^2}{N_1^2} \left(1 + \frac{R}{j\omega \frac{L_1}{N_{12}^2}} \right) \right)^{-1} = R \frac{N_1^2}{N_2^2} \left(1 + \frac{N_{12}^2 R}{j\omega L_1} \right)^{-1}$$


$$= N_{12}^2 R \left(1 + \frac{1}{j\omega \frac{L_1}{N_{12}^2 R}} \right)^{-1} = N_{12}^2 R \left(1 + \frac{1}{j\omega Z} \right)^{-1}$$

$$H(\omega) = \frac{V_{out}}{V_{in}} = \frac{\frac{j\omega L_1}{N_{12}^2}}{R + j\omega \frac{L_1}{N_{12}^2}} = \frac{j\omega \frac{L_1}{N_{12}^2 R}}{1 + j\omega \frac{L_1}{N_{12}^2 R}} = \left(1 + \frac{1}{j\omega \frac{L_1}{N_{12}^2 R}} \right)^{-1} = \left(1 + \frac{1}{j\omega Z} \right)^{-1}$$

therefore $Z_{in} = N_{12}^2 R H(\omega)$ where $H(\omega) = \left(1 + \frac{1}{j\omega Z} \right)^{-1}$

$\omega \gg \frac{2\pi}{Z}$, then $H(\omega)$ would approach 1 and Z_{in} would simplify to $Z_{in} = N_{12}^2 R$

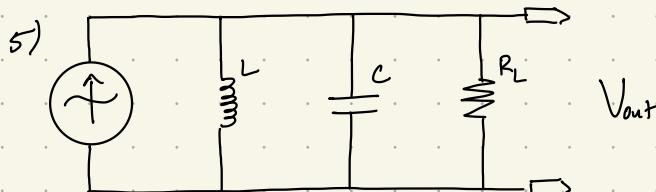$\omega \ll \frac{2\pi}{Z}$, then $H(\omega) = \left(1 + \frac{1}{j\omega Z} \right)^{-1} \approx j\omega Z$ and $Z_{in} = j\omega Z N_{12}^2 R$



$$a) Z_{tot} = \left(\frac{1}{j\omega L} + j\omega C + \frac{1}{R_L} \right)^{-1}$$

$$V_{out} = Z_{tot} I_o = I_o \left(\frac{1}{j\omega L} + j\omega C + \frac{1}{R_L} \right)^{-1}$$

$$H(\omega) = \frac{V_{out}}{I_o} = \left(\frac{1}{j\omega L} + j\omega C + \frac{1}{R_L} \right)^{-1} = \left(\frac{R_L + j\omega C (j\omega L) R_L + j\omega L}{j\omega L R} \right)^{-1}$$

$$= \left(\frac{R_L - \omega^2 L C R_L + j\omega L}{j\omega L R} \right)^{-1} = \frac{j\omega L R}{R_L - \omega^2 L C R_L + j\omega L}$$

$$= \frac{j\omega L R (R_L - \omega^2 L C R_L - j\omega L)}{(R_L - \omega^2 L C R_L + j\omega L)(R_L - \omega^2 L C R_L - j\omega L)} = \frac{\omega^2 L^2 R + j\omega L R (R_L - \omega^2 L C R_L)}{(R_L - \omega^2 L C R_L)^2 + \omega^2 L^2}$$

$$G(\omega) = |H(\omega)| = \sqrt{\left(\frac{\omega^2 L^2 R}{(R_L - \omega^2 L C R_L)^2 + \omega^2 L^2} \right)^2 + \left(\frac{\omega L R^2 (R_L - \omega^2 L C R_L)^2}{(R_L - \omega^2 L C R_L)^2 + \omega^2 L^2} \right)^2}^{1/2}$$

$$= \sqrt{\left(\frac{(\omega L R)^2 (\omega^2 L^2 + (R_L - \omega^2 L C R_L)^2)}{(R_L - \omega^2 L C R_L)^2 + \omega^2 L^2} \right)^2} = \frac{\omega L R}{\sqrt{\omega^2 L^2 + (R_L - \omega^2 L C R_L)^2}}$$

$$V_o = I_o \left(\frac{\omega^2 L^2 R + j\omega L R (R_L - \omega^2 L C R_L)}{(R_L - \omega^2 L C R_L)^2 + \omega^2 L^2} \right), \omega = \omega_0 = \frac{1}{\sqrt{L C}}$$

$$= I_o \left(\frac{\frac{L R}{C} + j \frac{R}{C} \sqrt{\frac{1}{C}} (R_L - R_c)}{(R_L - R_c)^2 + \frac{1}{C}} \right) = I_o \left(\frac{L R_c}{C} \cdot \frac{C}{R_L - R_c} \right) = I_o R_L$$

$$b) \frac{G(\omega)}{G(\omega_0)} = \frac{1}{\sqrt{2}} \Rightarrow G(\omega) = \frac{1}{\sqrt{2}} G(\omega_0)$$

$$G(\omega) = \frac{\omega L R_L}{\sqrt{\omega^2 L^2 + (R_L - \omega^2 L C R_L)^2}}, \quad G(\omega_0) = R_L, \quad BW = 2\Delta\omega = \omega_+ - \omega_-$$

$$\Rightarrow \sqrt{\omega^2 L^2 + (R_L - \omega^2 L C R_L)^2} = \frac{R_L}{\sqrt{2}} \Rightarrow \sqrt{\omega^2 L^2 + (R_L - \omega^2 L C R_L)^2} = \sqrt{2} \omega L$$

$$\omega^2 L^2 + (R_L - \omega^2 L C R_L)^2 = 2 \omega^2 L^2$$

$$(R_L - \omega^2 L C R_L)^2 = \omega^2 L^2$$

$$R_L - \omega^2 L C R_L = \pm \omega L$$

$$\Rightarrow \omega^2 L C R_L \pm \omega L - R_L = 0$$


$$\Rightarrow \omega^2 \pm \omega \frac{1}{C R_L} - \frac{1}{L C} = 0$$

$$\Rightarrow \omega_{\pm} = \frac{\pm \frac{1}{C R_L} + \sqrt{\frac{1}{C^2 R_L^2} + \frac{4}{L C}}}{2} = \pm \frac{1}{2 C R_L} + \frac{1}{2} \sqrt{\frac{1}{C^2 R_L^2} + \frac{4}{L C}} = \pm \frac{1}{2 C R_L} + \frac{1}{2 C R_L} \sqrt{1 + \frac{4 C R_L^2}{L}}$$


$$= \frac{1}{2 C R_L} \left(\sqrt{1 + \frac{4 C R_L^2}{L}} \pm 1 \right)$$

$$BW = \omega_+ - \omega_- = \frac{1}{2 C R_L} \left(\sqrt{1 + \frac{4 C R_L^2}{L}} + 1 - \sqrt{1 + \frac{4 C R_L^2}{L}} + 1 \right) = \underline{\frac{1}{C R_L}}$$
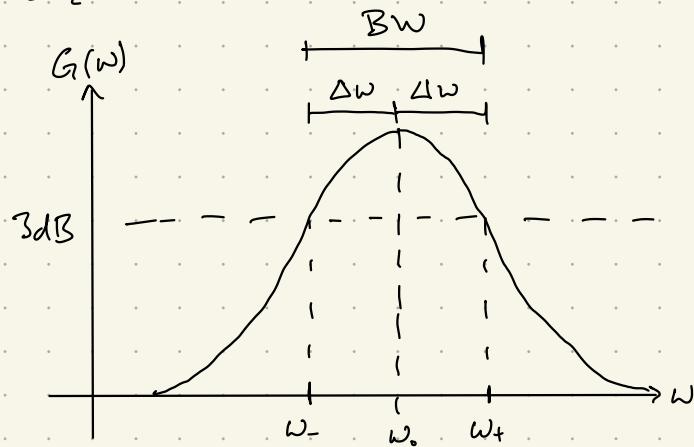
$$Q = \frac{\omega_0}{BW} = \omega R_L C = \frac{1}{\sqrt{LC}} R_L C = \underline{R_L \sqrt{\frac{C}{L}}}$$



6)

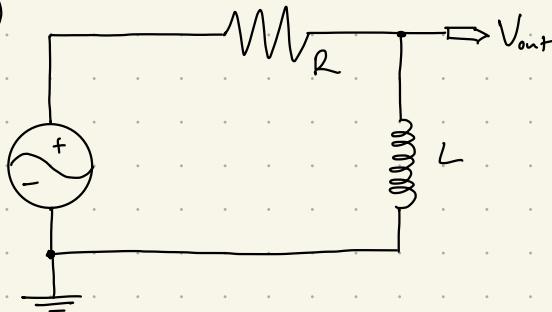

$$H(\omega) = \frac{V_{out}}{V_{in}} = \frac{j\omega L}{R + j\omega L} = \frac{j\omega \frac{L}{R}}{1 + j\omega \frac{L}{R}}, \quad \Sigma = \frac{L}{R}$$

$$= \frac{j\omega \Sigma}{1 + j\omega \Sigma} = \frac{j\omega \Sigma (1 - j\omega \Sigma)}{1 + \omega^2 \Sigma^2} = \frac{j\omega \Sigma + \omega^2 \Sigma^2}{1 + \omega^2 \Sigma^2}$$

$$G(\omega) = |H(\omega)| = \left| \frac{\omega^2 \Sigma^2 + j\omega \Sigma}{1 + \omega^2 \Sigma^2} \right| = \sqrt{\left(\frac{\omega^2 \Sigma^2}{1 + \omega^2 \Sigma^2} \right)^2 + \left(\frac{\omega \Sigma}{1 + \omega^2 \Sigma^2} \right)^2}$$

$$= \sqrt{\frac{(\omega \Sigma)^2 (1 + \omega^2 \Sigma^2)}{(1 + \omega^2 \Sigma^2)^2}} = \frac{\omega \Sigma}{\sqrt{1 + \omega^2 \Sigma^2}}$$

$$\varphi(\omega) = \tan^{-1}\left(\frac{\text{Im}[H(\omega)]}{\text{Re}[H(\omega)]}\right) = \tan^{-1}\left(\frac{\omega \Sigma}{1 + \omega^2 \Sigma^2} \cdot \frac{1 + \omega^2 \Sigma^2}{\omega \Sigma}\right) = \tan^{-1}\left(\frac{1}{\omega \Sigma}\right)$$

for RC high-pass filter: $\varphi(\omega) = \tan^{-1}\left(\frac{1}{\omega \Sigma}\right)$ and $G(\omega) = \frac{\omega \Sigma}{\sqrt{1 + \omega^2 \Sigma^2}}$ where $\Sigma = RC$


RL high-pass filter: $\varphi(\omega) = \tan^{-1}\left(\omega \Sigma\right)$ and $G(\omega) = \frac{\omega \Sigma}{\sqrt{1 + \omega^2 \Sigma^2}}$ where $\Sigma = \frac{L}{R}$

Therefore the RL and RC high pass have the exact same functional form.

$$G(\omega) = \frac{\omega \Sigma}{\sqrt{1 + \omega^2 \Sigma^2}} = \frac{1}{\sqrt{2}} \Rightarrow 2\omega^2 \Sigma^2 = 1 + \omega^2 \Sigma^2 \Rightarrow \omega^2 \Sigma^2 = 1 \Rightarrow \underline{\omega = \frac{1}{\Sigma}}$$

Lab Exercises:

Problem R2.1:

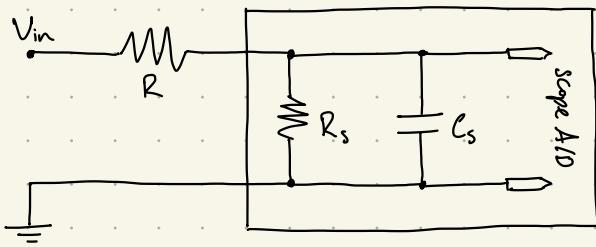


$$a) \omega_0 = \frac{2}{R_s C_s} \Rightarrow C_s = \frac{2}{\omega_0 R_s} = \frac{1}{\pi f_0 R_s}$$


$$R = R_s = 1 \text{ M}\Omega$$

$$f_0 = 5.9 \text{ kHz}$$

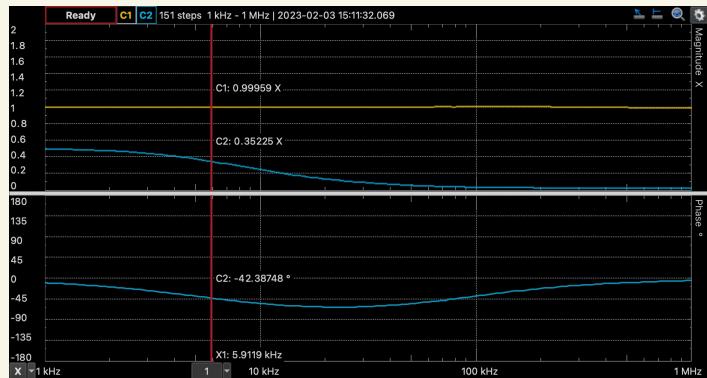
$$C_s = \frac{1}{\pi (5.9 \times 10^3) (1 \times 10^6)} = 5.39508 \times 10^{-11} \text{ F} = 53.95 \text{ pF}$$



b) $G(\omega)$ (X)

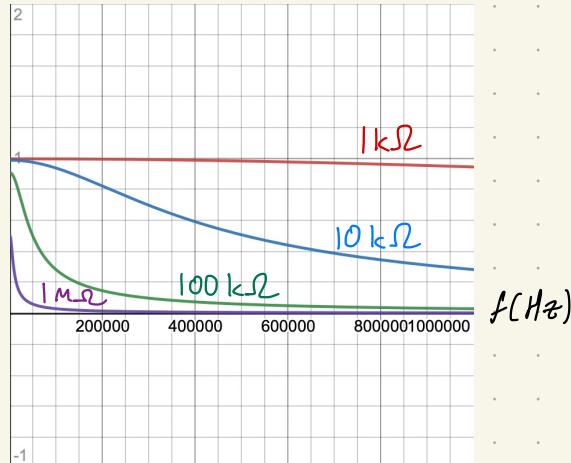

Problem R2.2

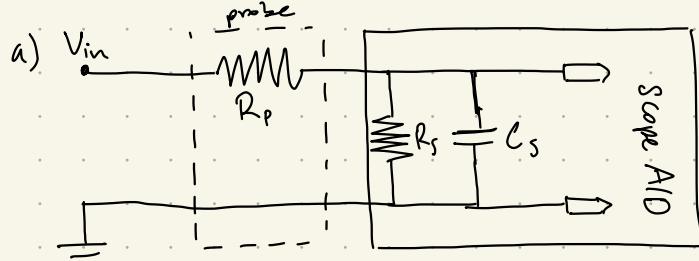


$$R_p = 2M\Omega$$

$$Z_{in} = R_p = 2 M\Omega$$

$$\omega_{3dB} = 4.4318 \text{ kHz}$$


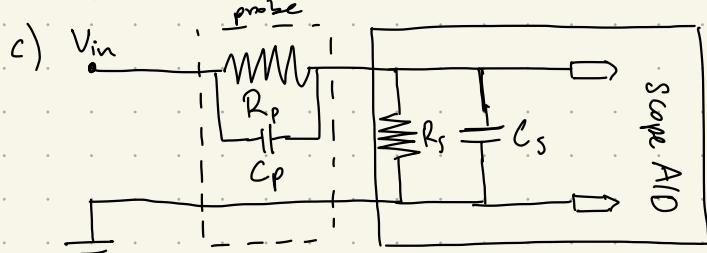
b) No, there is an observed distortion due to the charging and discharging of the capacitor, causing the scope to behave like a low-pass filter.



$$R_s = 1M\Omega, C_s = 54 \mu F$$

$$R \propto \frac{1}{C} \Rightarrow \frac{R_p}{C_s} = \frac{R_s}{C_p} \Rightarrow C_p = \frac{R_s}{R_p} C_s = \frac{1}{2} (54 \mu F) \approx 27 \mu F$$

$$\text{used } C_p = 23.5 \mu F$$

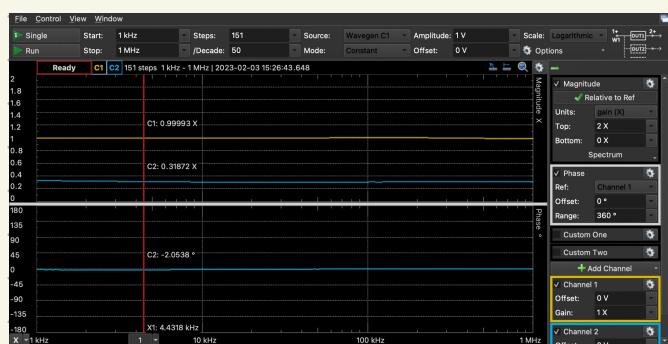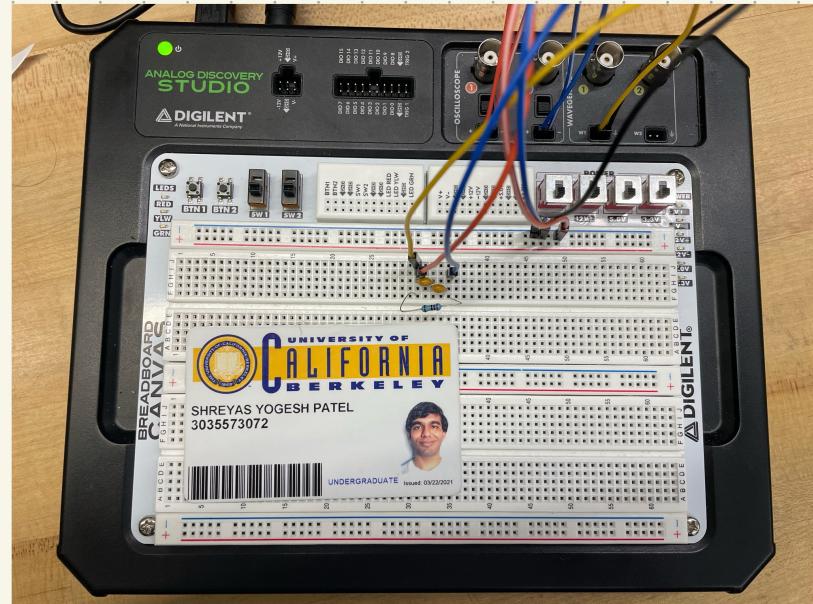


$$C_{tot} = \left(\frac{1}{C_1} + \frac{1}{C_2} \right)^{-1}$$


$$C_1 = C_2 = 47 \mu F$$

$$C_{tot} = 23.5 \mu F = C_p$$

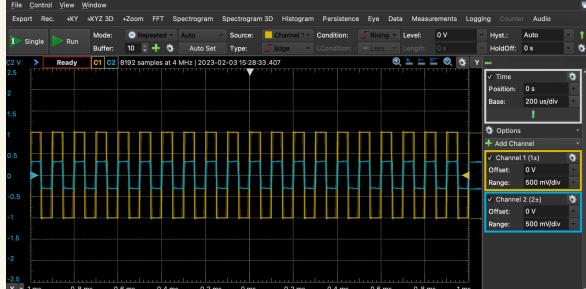d) The compensated probe recovers the original shape of the square input wave.



Problem R2.3

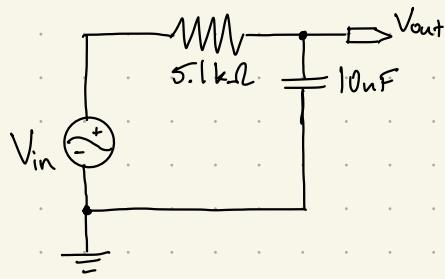

a) $f (\text{kHz}) | V_{peak \text{ before}} (\text{V}) | V_{peak \text{ after}} (\text{V})$

$f (\text{kHz})$	$V_{peak \text{ before}} (\text{V})$	$V_{peak \text{ after}} (\text{V})$
1	1.273	1.2077
3	0.43693	0.32396
5	0.28041	0.16245
7	0.22219	0.1088
9	0.20071	0.09048

b) $n | \text{Fourier coefficient} | V_{peak} (\text{V})$

n	$\text{Fourier coefficient}$	$V_{peak} (\text{V})$
1	1.273	1.273
3	0.424	0.437
5	0.255	0.280
7	0.182	0.222
9	0.141	0.201

The recorded peak voltages are close to their corresponding Fourier coefficients, but begin to diverge at higher frequencies/resonances.

c) Filtered coefficients are attenuated by a factor $A_n H(\omega)$ where A_n comes from the Fourier decomposition and $H(\omega)$ from the filter.

$$H(\omega) = \frac{1}{1+j\omega\tau} = \frac{1-j\omega\tau}{1+\omega^2\tau^2} = \frac{1}{1+\omega^2\tau^2} - j \frac{\omega\tau}{1+\omega^2\tau^2}, \quad \tau = 51 \mu\text{s}$$

n	Actual Attenuation	$H(\omega_n)$	$ H(\omega_n) $
1	0.9487	$0.91 - 0.286j$	0.954
3	0.7414	$0.53 - 0.499j$	0.728
5	0.5793	$0.288 - 0.453j$	0.5368
7	0.4897	$0.171 - 0.377j$	0.414
9	0.4508	$0.111 - 0.314j$	0.333

<u>n</u>	<u>Pre-Lab Calc</u>	<u>Un-filtered Fourier Coefficients</u>	
1	0.5	0.637	0.8079
2	0.398	0.322	0.0885
3	0.265	0.218	0.0312
4	0.0997	0.169	0.0154
5	0.0639	0.141	0.0087

ramp

triangle

The harmonics for the triangle wave were at odd integer values while they were at even harmonics for the ramp wave.

Problem R2.4

a) low-pass filter: $G(\omega) = \frac{1}{\sqrt{1+\omega^2C^2}} = \frac{V_{out}}{V_{in}} \Rightarrow \left(\frac{V_{in}}{V_{out}}\right)^2 = 1 + \omega^2 C^2 \Rightarrow C = \frac{1}{\omega} \left(\left(\frac{V_{in}}{V_{out}} \right)^2 - 1 \right)^{1/2}$

$$V_{in} = 0.99256 \text{ V}$$

$$V_{out} = 46.414 \text{ mV}$$

$$RC = C = \frac{1}{2\pi f} \left(\frac{V_{in}}{V_{out}} - 1 \right) = \frac{1}{2\pi(50 \text{ Hz})} \left(\left(\frac{0.99256 \text{ V}}{46.414 \text{ mV}} \right)^2 - 1 \right)^{1/2} = 6.8 \mu\text{s}$$

b) high-pass filter: $G(\omega) = \frac{\omega C}{\sqrt{1+\omega^2C^2}} = \frac{V_{out}}{V_{in}} \Rightarrow \omega^2 C^2 = \left(\frac{V_{out}}{V_{in}} \right)^2 (1 + \omega^2 C^2) \Rightarrow \omega^2 C^2 \left(1 - \left(\frac{V_{out}}{V_{in}} \right)^2 \right) = \left(\frac{V_{out}}{V_{in}} \right)^2$

$$V_{in} = 0.99239 \text{ V}$$


$$V_{out} = 0.98176 \text{ V}$$

$$RC = C = \frac{1}{2\pi f} \left(\frac{V_{out}}{V_{in}} \right) \left(1 - \left(\frac{V_{out}}{V_{in}} \right)^2 \right)^{-1/2} = 21.57 \mu\text{s}$$

Problem R2.5

a) $f = 10 \text{ kHz}$, $L = 2.577 \text{ mH}$

b)

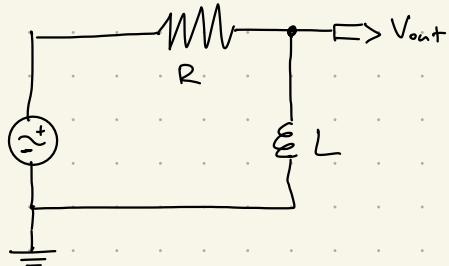

$$G(\omega) = \frac{\omega Z}{\sqrt{1 + \omega^2 Z^2}} = \frac{1}{\sqrt{2}}, \quad Z = \frac{L}{R}$$

$$2\omega^2 Z^2 = 1 + \omega^2 Z^2$$

$$\omega^2 Z^2 = 1$$


$$\omega = \frac{1}{Z} = \frac{R}{L} \Rightarrow R = \omega L = 2\pi f L$$

$$R = 2\pi(11 \text{ kHz})(2.577 \text{ mH}) = 178.109 \Omega$$

We used $100\Omega, 68\Omega, 10\Omega$ resistors in series

The measured 3dB is 10.835 kHz which agrees with our design.

Problem R2.6

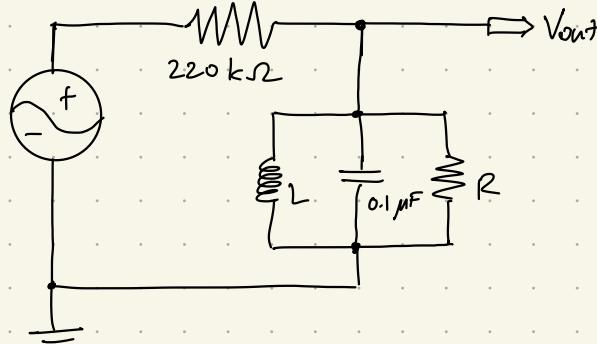

$$a) f_o = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{(2.577 \text{ mH})(0.1 \mu\text{F})}} = 9.914 \text{ kHz}$$

$$b) R = 10 \text{ k}\Omega$$

$$f = 10.285 \text{ kHz}$$

This measurement is within 4% of our expectations

$$2 \times 0.208$$

$$c) Q = \frac{f_o}{BW}, \quad f_{3\text{dB}} = 10.493 \text{ kHz} \Rightarrow BW = 2(10.493 - 10.285) = 0.416 \text{ kHz}$$

$$Q = \frac{10.285}{0.416} = 24.72$$

$$d) R = 1 \text{ k}\Omega, \quad f_o = 10.326 \text{ kHz}, \quad f_{3\text{dB}} = 11.370 \text{ kHz} \Rightarrow BW = 2.058 \Rightarrow Q = 5.05$$

$$R = 3 \text{ k}\Omega, \quad f_o = 10.326 \text{ kHz}, \quad f_{3\text{dB}} = 10.706 \text{ kHz} \Rightarrow BW = 0.760 \Rightarrow Q = 13.59$$

$$e) Q = R\sqrt{\frac{C}{L}} = R\sqrt{\frac{0.1 \mu\text{F}}{2.577 \text{ mH}}} = 0.00623 R$$


$$R = 10 \text{ k}\Omega, \quad Q = 62.29$$

$$R = 1 \text{ k}\Omega, \quad Q = 6.23$$

$$R = 3 \text{ k}\Omega, \quad Q = 18.69$$

at higher resistances, the Q factor diverges, where the ideal is higher than actual.

f)

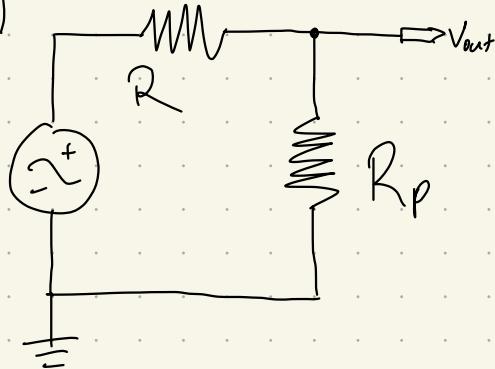

$$V_{out} = V_o \frac{R_p}{R_s + R_p} \Rightarrow (R_s + R_p) \frac{V_{out}}{V_o} = R_p$$

$$\Rightarrow \frac{V_{out}}{V_o} R_s = (1 - \frac{V_{out}}{V_o}) R_p \quad (R_s + R_p) \frac{V_{out}}{V_o} = R_s$$

$$\Rightarrow R_p = (1 - \frac{V_{out}}{V_o})^{-1} \frac{V_{out}}{V_o} R_s \quad \frac{V_{out}}{V_o} R_p = (1 - \frac{V_{out}}{V_o}) R_s$$

$$\frac{V_{out}}{V_o} = 0.06261$$

$$R_p = (1 - \frac{V_{out}}{V_o}) \frac{V_o}{V_s} R_s \quad 3.7 \text{ m}\Omega$$

$$R_p = (1 - 0.06261)^{-1} (0.06261) (220 \text{ k}\Omega)$$

$$= 14.69 \text{ k}\Omega$$

g) $f_o = 10.574 \text{ kHz}$, $f_{3dB} = 10.648 \text{ kHz} \Rightarrow \text{BW} = 0.148$

$$\Rightarrow Q = 71.45$$

$$Q = R_p \sqrt{\frac{C}{L}} = 91.52$$


The measured Q is same order of magnitude as the theoretical Q , but the value is much lower

$R = 1 \text{ k}\Omega$, $R_{tot} = 936.27 \text{ }\Omega$, $Q = 5.83$

$R = 3 \text{ k}\Omega$, $R_{tot} = 2.491 \text{ k}\Omega$, $Q = 15.52$

$R = 10 \text{ k}\Omega$, $R_{tot} = 5.95 \text{ k}\Omega$, $Q = 37.07$

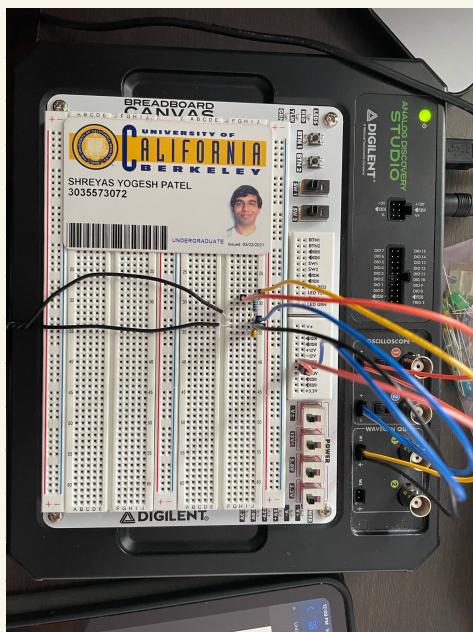These values are closer to the measured values, but still greater and diverge at higher values of R .



The inductor is just
barely offscreen, but
the black wires are its leads.
It can be seen in full in the
picture on the next page.

Problem R2.7

a) $f = 10 \text{ kHz}$, $L = 104.8 \mu\text{H}$

b) $L = \mu_0 K N^2 \frac{A}{l} \Rightarrow \frac{L_1}{L_2} = \frac{N_1^2}{N_2^2} = \frac{25^2}{5^2} = 25$

$$\frac{L_1}{L_2} = \frac{2.577 \text{ mH}}{104.8 \mu\text{H}} = 24.59$$


The ratio agrees with our theoretical expectations.

c) $Z_L = j\omega L$, $\omega = 2\pi f \Rightarrow Z_L = 2\pi j f L$


$f = 1 \text{ kHz}$, $Z_L = 0.658 j$

$f = 10 \text{ kHz}$, $Z_L = 6.58 j$

$f = 100 \text{ kHz}$, $Z_L = 65.8 j$

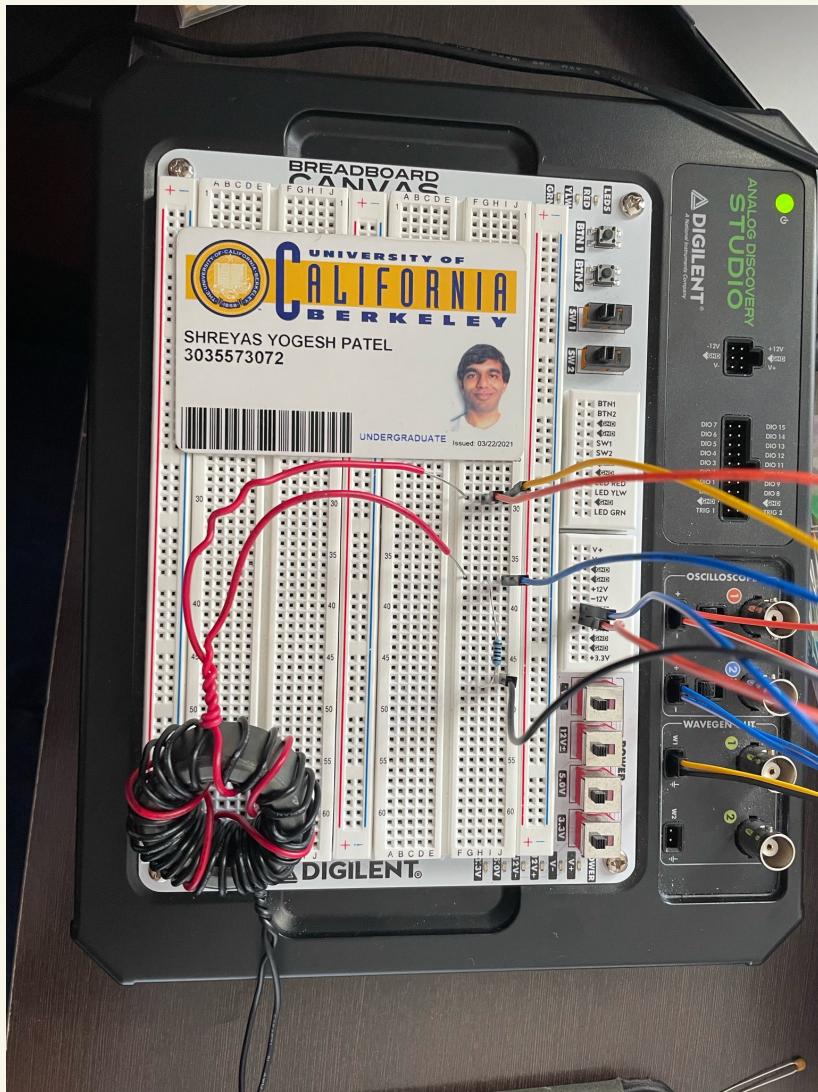

Problem R2.8

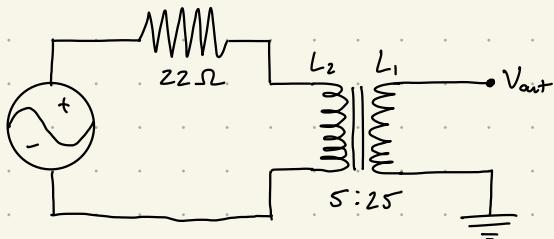


step-up transformer

$$a) \text{ theoretical: } \frac{V_1}{V_2} = \frac{25}{5} = 5$$

$$\text{measured: } \frac{V_1}{V_2} = \frac{2.7551}{0.705} = 3.9$$

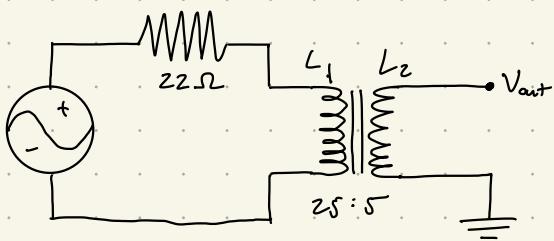The values are close but have a 28% difference.



step-down transformer

$$b) \text{ theoretical: } \frac{V_2}{V_1} = \frac{5}{25} = 0.2$$

$$\text{measured: } \frac{V_2}{V_1} = \frac{0.1996}{1.0058} = 0.1996$$

The measured ratio is almost the same as the theoretical.

$$c) k = \sqrt{V_{12} V_{21}}, N_{21} = \sqrt{\frac{V_{21}}{V_{12}}} \Rightarrow N_{12} = \sqrt{\frac{V_{12}}{V_{21}}}$$

$$N_{12} = \left(\frac{V_{12}}{V_{21}} \right)^{1/2} = \left(\frac{3.9}{0.1996} \right)^{1/2} = 4.42$$

$$k = ((3.9)(0.1996))^{1/2} = 0.882$$


$$d) I = \frac{V}{R} = \frac{13.9 \text{ mV}}{22 \Omega} = 0.632 \text{ mA}$$

$$Z_{\text{primary}} = \frac{V}{I} = \frac{1.0051 \text{ V}}{0.632 \text{ mA}} = 1.59 \text{ k}\Omega$$

$$Z_{\text{exp}} = 2\pi(100 \text{ kHz})(2.577 \text{ mH})j = 1.62j \text{ k}\Omega$$

The value agrees with the expectation value.

e)

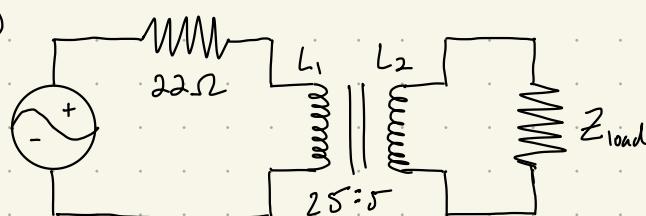

$$Z_{L1} \gg Z_{\text{load}}$$

$$2\pi f L \gg Z_{\text{load}} \Rightarrow (100 \text{ kHz})(104.8 \mu\text{H}) = 65.85 \Omega \gg Z_{\text{load}}$$

$$\underline{Z_{\text{load}} \ll 65.85 \Omega}$$

$$f) \frac{V_2}{V_1} = \frac{125.45 \text{ mV}}{0.63280 \text{ V}} = 0.198$$

The ratio is not different.

$$g) I_1 = \frac{V}{R} = \frac{113.17 \text{ mV}}{22 \Omega} = 5.14 \text{ mA}$$

$$Z_{\text{primary}} = \frac{V}{I} = \frac{0.63449 \text{ V}}{5.14 \text{ mA}} = 123 \Omega$$

Z_{load} has a voltage drop across it, and the transformer maintains the step-down ratio, so there is less of a drop across L_1 , since L_2 also has a lower potential drop across it.

h) with 4.7Ω resistor: $\Delta t = 164.16 \text{ ns} \Rightarrow \Delta \omega = 2\pi \frac{\Delta t}{T} = 2\pi \frac{164.16 \text{ ns}}{99.726 \text{ ns}} = 0.103$

Floating leads: $\Delta t = 1.4364 \mu\text{s} \Rightarrow T = 10.096 \mu\text{s} \Rightarrow \Delta \omega = 2\pi \frac{1.4364}{10.096} = 0.894$

$0.33 \mu\text{F}$ capacitor: $\Delta t = 2.4213 \mu\text{s} \Rightarrow T = 9.9316 \mu\text{s} \Rightarrow \Delta \omega = 2\pi \frac{2.4213}{9.9316} = 1.532$

The greater the impedance of the load, the smaller the phase difference becomes

$$i) I_2 = \frac{124.11 \text{ mV}}{4.7 \Omega} = 26.41 \text{ mA}$$

$$\frac{I_2}{I_1} = \frac{26.41 \text{ mA}}{5.14 \text{ mA}} = 5.14$$

$$0 = -j\omega M I_1 + j\omega L_2 I_2 + Z_L I_2$$

$$j\omega M \left(\frac{I_1}{I_2} \right) = j\omega L_2 + Z_L$$

$$\frac{I_1}{I_2} = \frac{j\omega L_2 + Z_L}{j\omega M} \Rightarrow \frac{j\omega k\sqrt{L_1 L_2}}{j\omega L_2 + Z_L} = \frac{I_1}{I_2} = \frac{2\pi (100 \text{ mH})(0.882) \sqrt{(104.8 \mu\text{H})(2.522 \mu\text{H})}}{2\pi (100 \text{ mH})(104.8 \mu\text{H})} = 4.08$$

The current ratio is comparable to the expected ratio

Problem R2.9

a) $R = 10 \text{ k}\Omega$

$$f_o = 9.9189 \text{ kHz}, f_{3\text{dB}} = 9.9950 \text{ kHz} \Rightarrow BW = 0.1522 \Rightarrow Q = 65.17$$

$$R = 100 \text{ k}\Omega$$

$$f_o = 9.9141 \text{ kHz}, f_{3\text{dB}} = 9.9223 \text{ kHz} \Rightarrow BW = 0.0164 \Rightarrow Q = 604.52$$

b) $R = 10 \text{ k}\Omega$

$$f_o = 9.9189 \text{ kHz}, f_{3\text{dB}} = 9.9970 \text{ kHz} \Rightarrow BW = 0.1562 \Rightarrow Q = 63.5$$

$$Q_{\text{exp}} = R \sqrt{\frac{C}{L}} = (10 \text{ k}\Omega) (0.1 \mu\text{F} / 2.577 \text{ mH})^{1/2} = 62.29$$

$$R = 100 \text{ k}\Omega$$

$$f_o = 9.9149 \text{ kHz}, f_{3\text{dB}} = 9.9262 \text{ kHz} \Rightarrow BW = 0.0226 \Rightarrow Q = 438.7$$

$$Q_{\text{exp}} = 622.94$$

The actual Q is close to expected at low R_{load} , but diverges to lower values at higher R_{load} values.

c) $R = 1 \text{ k}\Omega$

$$f_o = 9.9189 \text{ kHz}, f_{3\text{dB}} = 10.811 \text{ kHz} \Rightarrow BW = 1.7842 \text{ kHz} \Rightarrow Q = 5.56$$

$$R = 3 \text{ k}\Omega$$

$$f_o = 9.9189 \text{ kHz}, f_{3\text{dB}} = 10.243 \text{ kHz} \Rightarrow BW = 0.6482 \text{ kHz} \Rightarrow Q = 15.3$$

$$R = 10 \text{ k}\Omega$$

$$f_o = 9.9149 \text{ kHz}, f_{3\text{dB}} = 10.053 \text{ kHz} \Rightarrow BW = 0.2762 \text{ kHz} \Rightarrow Q = 35.898$$

These Q values are close, but still greater than the recorded values, diverging at higher values of R .