


# Physics 111A Lab 6


## Pre-Lab Questions

- 1) To ensure the input draws no current, or for it to be approximated doing so, the frequency of any AC current must be much less than 1 MHz to ensure the input impedance from the  $\sim 3\text{ pF}$  capacitor is very high. These same limitations are applied to ensure the second golden rule where the voltage difference between the two inputs is as close to zero as possible. You also need the output to feedback to the negative input.


The LF356 deviates from ideal when used in a follower because there is a small error voltage between inputs causing the magnitude of the output voltage to be slightly less than the input.

- 2)  $Z_{out}$  of an ideal op-amp follower is 0.

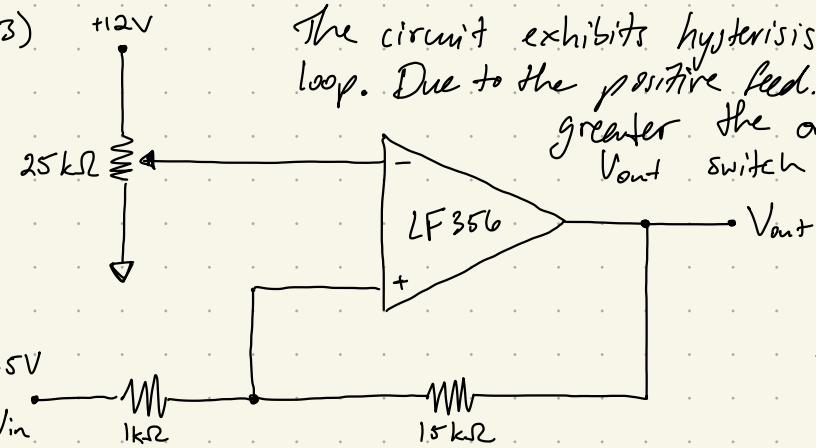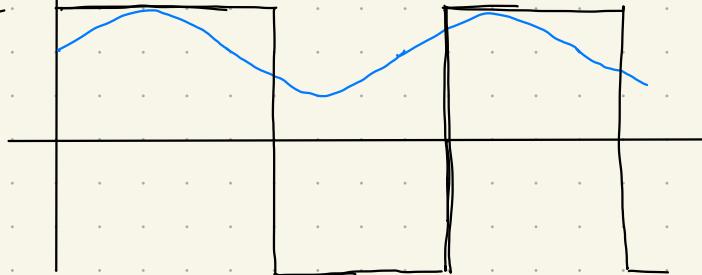- 3) 
 The circuit exhibits hysteresis because it is set up as a positive feedback loop. Due to the positive feedback loop,  $V_{in}$  has to become more greater than or less than  $V_c$  for  $V_+ - V_- = 0$  to make  $V_{out}$  switch in sign.


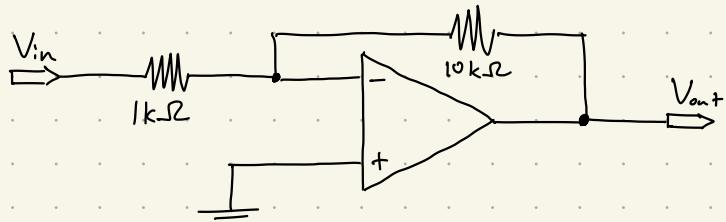
$$4) G_C = -\frac{R_2}{R_1}, \quad R_1 = 1\text{k}\Omega, \quad \Rightarrow G_C = -\frac{R_2}{R_1} = -10 \Rightarrow R_2 = 10\text{k}\Omega$$




$$5) R_1 = 1\text{k}\Omega, \quad R_2 = 2\text{k}\Omega, \quad G_C = 1 + \frac{R_2}{R_1} = 1 + \frac{2\text{k}\Omega}{1\text{k}\Omega} = 3 \quad V_{in} \quad \underline{\hspace{1cm}}$$

- 6) It is an ideal current to voltage converter because the op-amps inputs draw no current, and it goes entirely into the resistor.

$$V_{out} = I_{in} R$$

5) continued

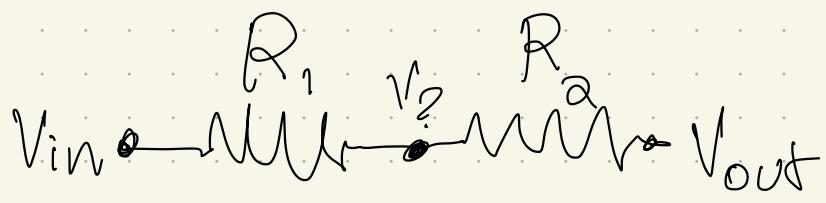

$$I = \frac{V_{out} - V_{in}}{R_1 + R_2} = \frac{V_{out} - V_{in}}{R_1}$$

$$\frac{R_1(V_{out} - V_{in})}{R_1 + R_2} + V_{in} = V_1$$

$$V_1 = V_{in} \left( \frac{R_2}{R_1 + R_2} \right) + V_{out} \left( \frac{R_1}{R_1 + R_2} \right)$$

$$= \frac{V_{in} R_2 + V_{out} R_1}{R_1 + R_2} = 0$$

$$V_{in} R_2 = -V_{out} R_1$$


$$V_{in} = -V_{out} \frac{R_1}{R_2}$$

$$V_2 - V_{in} = \frac{R_1}{R_1 + R_2} (V_{out} - V_{in})$$

$$\frac{V_2 - V_{in}}{V_{out} - V_{in}} = \frac{R_1}{R_1 + R_2}$$

# Lab Exercises:


## Problem R6.1:

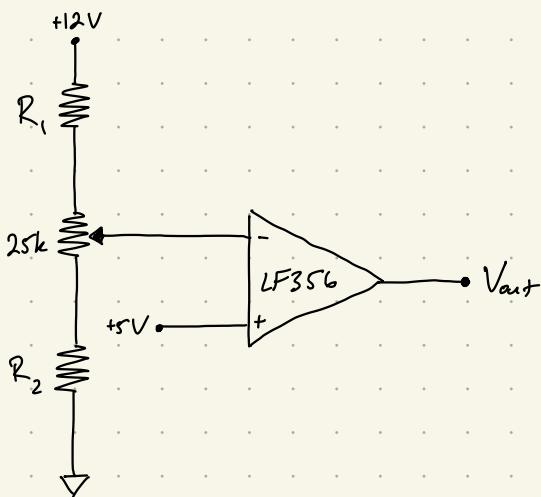

Voltages intermediate to  $\pm 10.5V$  are very hard to acquire because the change between the two is near instantaneous.

lower bound  $G_L \approx 2.1$

## Problem R6.2

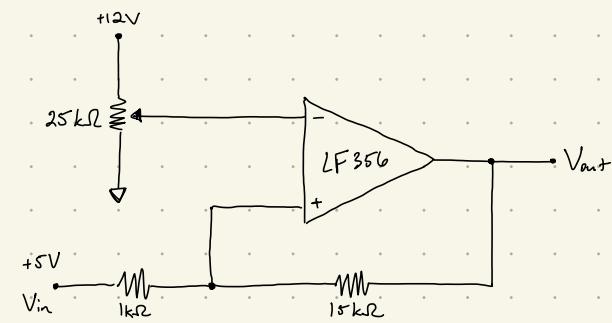

a)



$$b) V_{\text{thresh}} = V_- \left(1 + \frac{R_1}{R_2}\right) = 0$$

$$\text{low} \rightarrow \text{high} : V_{\text{in}} = 1.0024V$$

$$\text{theoretical } V_{\text{in}} = \frac{R_1}{R_2} V_{\text{out}} = \frac{1k\Omega}{15k\Omega} (11.3V) = 0.753V$$

$$\text{high} \rightarrow \text{low} : V_{\text{in}} = -0.9024V$$

$$\text{theoretical } V_{\text{in}} = -\frac{R_1}{R_2} V_{\text{out}} = -\frac{1k\Omega}{15k\Omega} (10.5V) = 0.7V$$

$$c) V_{\text{thresh}} = V_- \left(1 + \frac{R_1}{R_2}\right) = 3.52V$$



$$\text{low} \rightarrow \text{high} : V_{\text{in}} = 4.3357V$$

$$\text{theoretical } V_{\text{in}} = V_{\text{thresh}} + \frac{R_1}{R_2} V_{\text{out}} = 3.52V + \frac{1}{15}(11.2V) = 4.27V$$


$$\text{high} \rightarrow \text{low} : V_{\text{in}} = 2.55V$$

$$\text{theoretical } V_{\text{in}} = V_{\text{thresh}} - \frac{R_1}{R_2} V_{\text{out}} = 3.52V - \frac{1}{15}(10.5V) = 2.82V$$

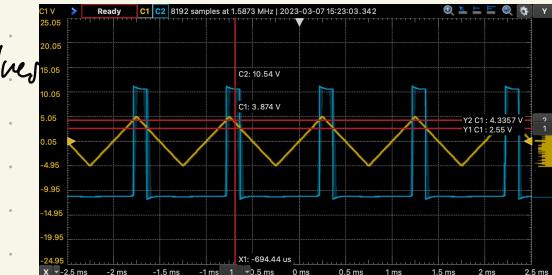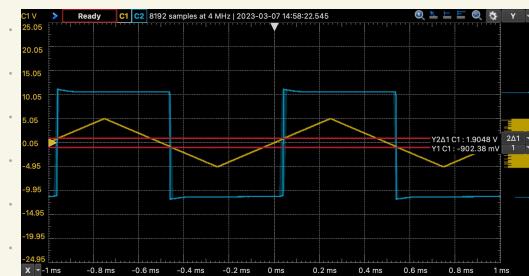the transition voltages are fairly close to the calculated values



### Problem R6.3

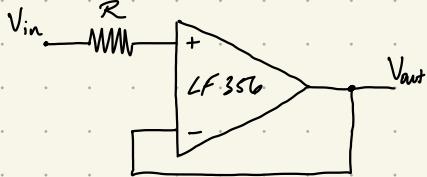

a)  $R = 0$ , 1MHz square wave

$V_{in} = 0.1 \text{ V}$ ,  $V_{out}$  fluctuates between  $-20 \text{ mV}$  and  $20 \text{ mV}$

$V_{in} = 0.2 \text{ V}$ ,  $V_{out}$  fluctuates between  $-40 \text{ mV}$  and  $40 \text{ mV}$

$V_{in} = 1 \text{ V}$ ,  $V_{out}$  fluctuates between  $-160 \text{ mV}$  and  $230 \text{ mV}$

$V_{in} = 2 \text{ V}$ ,  $-180 \text{ mV} \leq V_{out} \leq 608 \text{ mV}$

$V_{in} = 5 \text{ V}$ ,  $2 \text{ V} \leq V_{out} \leq 3 \text{ V}$


b)  $R = 5.6 \text{ M}\Omega$ ,  $f_{zad} = 3.2713 \text{ kHz}$

$$\phi = 137.77^\circ$$

c)  $f_{zad} = \frac{1}{2\pi RC} \Rightarrow C = (2\pi (3.2713 \text{ kHz}) (5.6 \text{ M}\Omega))^{-1}$

$C = 8.687 \text{ pF} > 3 \text{ pF}$  due to parasitic oscillations

### Problem R6.4

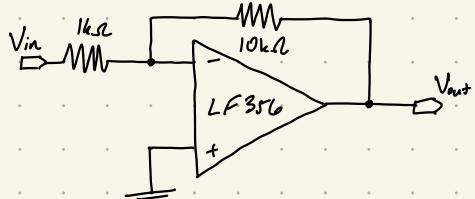

a) 1kHz 0.1 V sine wave  $G = \frac{0.95 \text{ V}}{94.62 \text{ mV}} = 10.0401$

$$R_1 = 0.996 \text{ k}\Omega, R_2 = 9.91 \text{ k}\Omega$$

$$V_{in} = 94.62 \text{ mV}$$

$$\text{expected } G_c = \frac{9.91}{0.996} = 9.95$$

b) amplitude 100mV

$$f_{zad} = 545 \text{ kHz}$$


c)  $R_2 = 100 \text{ k}\Omega$  for  $G \sim 100$ ,  $V = 10 \text{ mV}$

$$f_{zad} = 55.23 \text{ kHz}$$

d)  $G = 10.04$ ,  $f_{zad} = 545 \text{ kHz} \Rightarrow 5.4 \text{ MHz}$

$$G = 100, f = 55.23 \text{ kHz} \Rightarrow 5.523 \text{ MHz}$$

### Problem R6.5

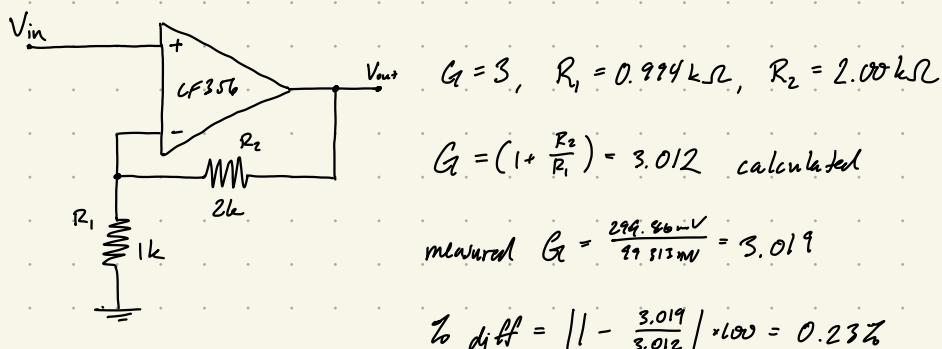

$$G = 3, R_1 = 0.994 \text{ k}\Omega, R_2 = 2.004 \text{ k}\Omega$$

$$G = \left(1 + \frac{R_2}{R_1}\right) = 3.012 \text{ calculated}$$

$$\text{measured } G_c = \frac{299.86 \text{ mV}}{99.813 \text{ mV}} = 3.019$$

$$\% \text{ diff} = \left| 1 - \frac{3.019}{3.012} \right| \times 100 = 0.23\%$$

### Problem R6.6

$$I_{out} = \frac{V}{I}, V_{out} = -G_o V$$

$$V_+ = \frac{4.7k\Omega}{4.7k\Omega + 470k\Omega} V = 0.091V \approx V_{out} = -G_o (0.091V)$$

$$I_{10k} = \frac{V_s - V_{out}}{10k\Omega} = \frac{V_s + G_o (0.091V)}{10k\Omega}$$


$$I_{470k} = \frac{V_s - V_+}{470k\Omega} = \frac{V_s - 0.091V}{470k\Omega}$$

$$I_{total} = \frac{V_s + G_o (0.091V)}{10k\Omega} + \frac{V_s - 0.091V}{470k\Omega} = \frac{470k\Omega (V_s + G_o (0.091V)) + 10k\Omega (V_s - 0.091V)}{470k\Omega} = \frac{470k\Omega V_s + 470k\Omega \cdot 0.091V G_o + 10k\Omega V_s - 0.091V}{470k\Omega} = \frac{57k\Omega V_s + (47k\Omega \cdot G_o - 10k\Omega) 0.091V}{470k\Omega}$$

$$I_{out} = \frac{V_s}{I_{tot}} = \frac{470k\Omega V_s}{57k\Omega V_s + (47k\Omega \cdot G_o - 10k\Omega) 0.091V}$$

$$Z_{out} \approx \frac{470k\Omega}{57k\Omega V_s + 47k\Omega \cdot G_o \cdot 0.091V} \text{ and } G_o \text{ is very large}$$

### Problem R6.7

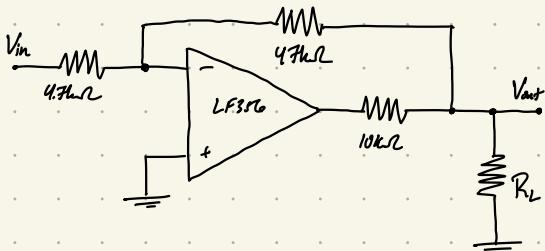

1kHz sine wave


w/  $R_L$   
w/o  $R_L$

Vin amplitude 0.1V	Vin amplitude 0.5V
-9.629	-1.929
-10.019	-9.919

with  $R_L$ , distortion appears at the peak of the output signal  
when  $V_{in}$  is increased to 0.5V the output resembles a square wave

A gain of -10 is expected for the inverting amplifier except when  $V_{in} = 0.5V$  and  $R_L$  is in place.  $V_{out}$  would have to be 5V to keep this true which would need a current of 5mA.


### Problem R6.8

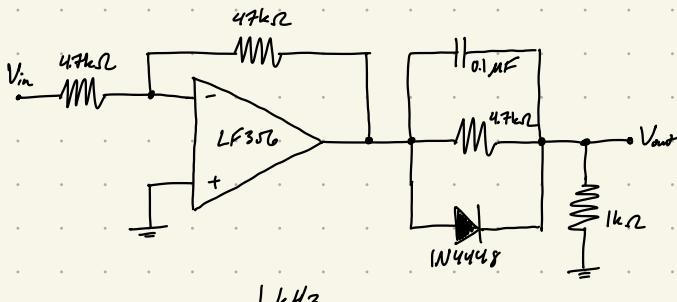


Distortion seen at 10kHz and 100Hz

The charging and discharging of the capacitor contributes to this while other distortions are frequency dependent.


0.1V

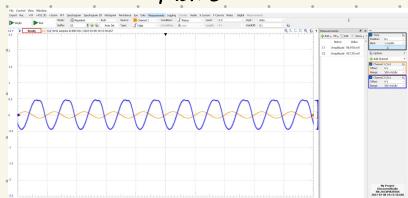




10kHz

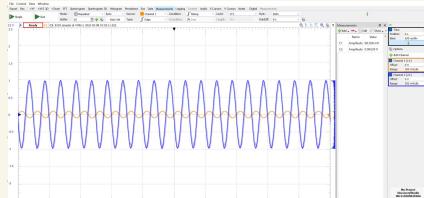


100Hz

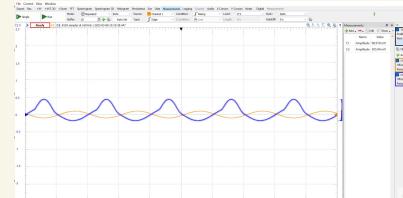


0.5V

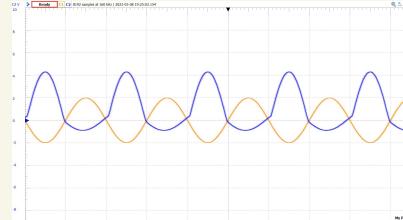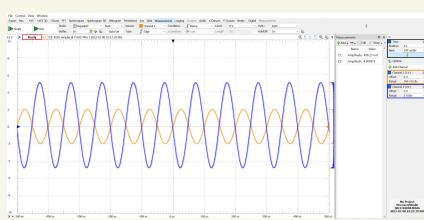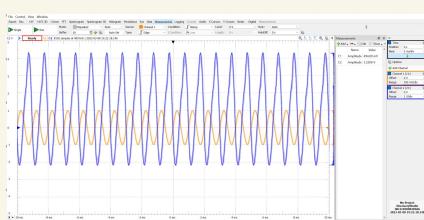


# Problem R6.9

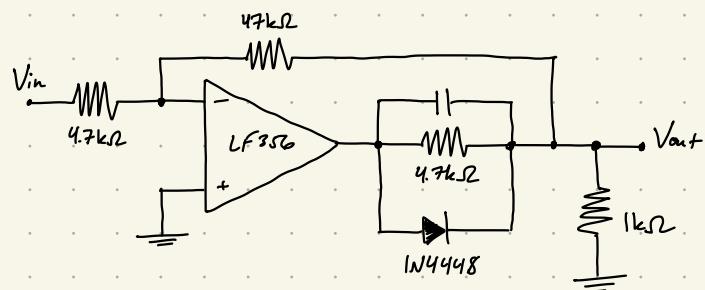

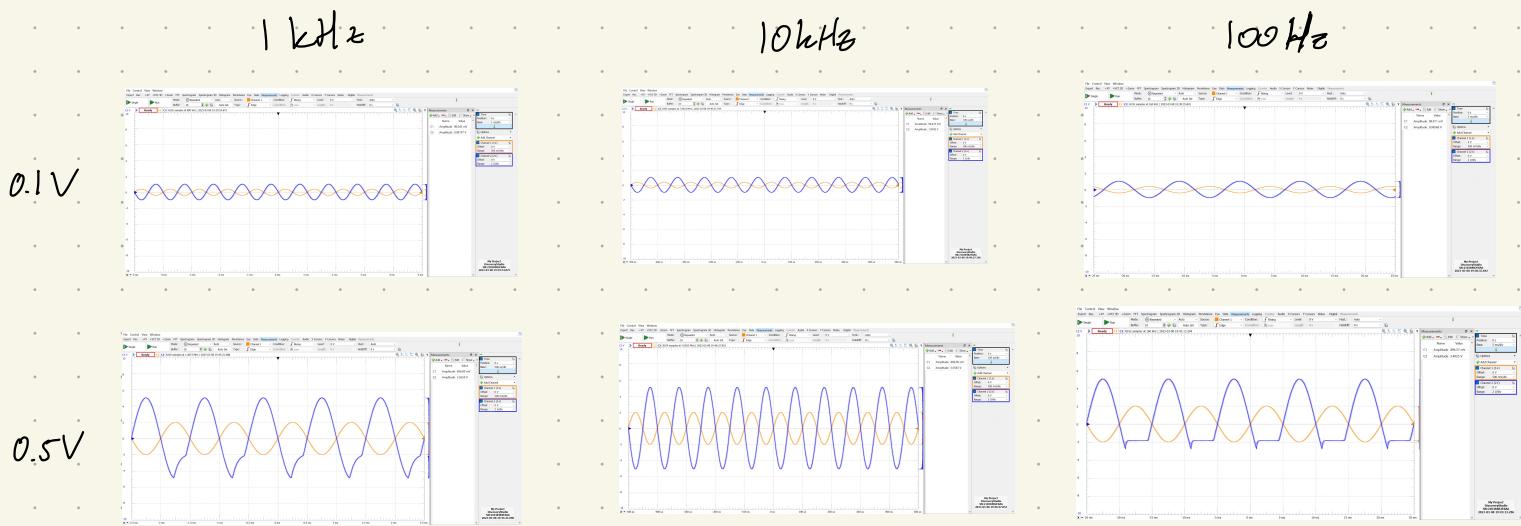Conducting the same investigation as the previous part, we see that frequency dependent distortions for 0.1V are removed. The distortions are still present when the amplitude is 0.5V at low frequencies.



### Problem R6.10

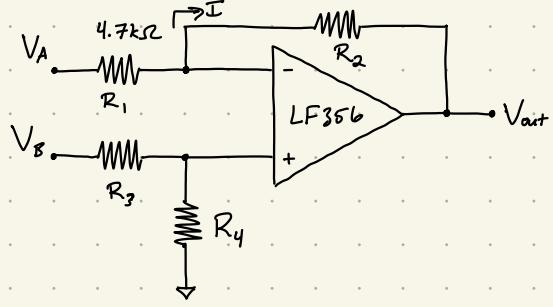

$$V_A = -12V$$

$$V_B = 12V$$

$$a) V_- = \frac{V_A R_2 + V_{out} R_1}{R_1 + R_2}$$

$$V_t = V_B \left( \frac{R_4}{R_3 + R_4} \right)$$

$$I = \frac{V_{out} - V_-}{R_2} = \frac{V_- - V_A}{R_1} \Rightarrow V_{out} = \frac{R_2}{R_1} (V_- - V_A) + V_- = \left( \frac{R_1 + R_2}{R_1} \right) V_- - \frac{R_2}{R_1} V_A, V_- = V_+$$

$$V_{out} = \left( \frac{R_1 + R_2}{R_1} \right) V_- - \frac{R_2}{R_1} V_A = \left( \frac{R_1 + R_2}{R_1} \right) \left( \frac{R_4}{R_3 + R_4} \right) V_B - \frac{R_2}{R_1} V_A = \frac{R_4 (R_1 + R_2)}{R_1 (R_3 + R_4)} V_B - \frac{R_2}{R_1} V_A = 0$$

$$\frac{R_4}{R_1} \frac{R_1 + R_2}{R_3 + R_4} V_B = \frac{R_2}{R_1} V_A \Rightarrow \frac{R_4}{R_2} \frac{R_1 + R_2}{R_3 + R_4} V_B = V_A$$

$$V_{out} = 10(V_B - V_A) = 10V_B - 10V_A = \frac{R_4 (R_1 + R_2)}{R_1 (R_3 + R_4)} V_B - \frac{R_2}{R_1} V_A$$

$$\frac{R_2}{R_1} = 10 \Rightarrow R_2 = 10R_1, \frac{R_4 (R_1 + R_2)}{R_1 (R_3 + R_4)} = 10 \Rightarrow \frac{R_4 (11R_1)}{R_1 (R_3 + R_4)} = 10 \Rightarrow 11R_4 = 10R_3 + 10R_4 \Rightarrow R_4 = 10R_3$$

$$V_{out} = 10(V_B - V_A) = 0 \Rightarrow V_A = V_B$$

$$\frac{R_4 (R_1 + R_2)}{R_1 (R_3 + R_4)} V_B - \frac{R_2}{R_1} V_A = 0 \Rightarrow \frac{R_4 (R_1 + R_2)}{R_1 (R_3 + R_4)} = \frac{R_2}{R_1} \Rightarrow \frac{R_4 (11R_1)}{R_1 (11R_3)} = \frac{R_2}{R_1} \Rightarrow \frac{R_4}{R_2} = \frac{R_2}{R_3} \Rightarrow \frac{R_4}{R_2} = \frac{R_2}{R_1}$$

$$R_1 = R_3, R_2 = R_4 = 10R_1$$

$$R_1 = R_3 = 4.7k\Omega, R_2 = R_4 = 47k\Omega$$

$$V_+ = V_- = 523.8mV, V_{out} = 22.26mV$$


$$V_C = \frac{1}{2}(V_+ + V_-) = \frac{1}{2}(523.8 + 523.8) = 523.8mV$$

$$G_C = \frac{22.26mV}{523.8mV} = 0.04$$

$V_A$  grounded:  $V_+ = 1.0005V, V_{out} = 9.8704V, G = \frac{V_{out}}{V_+} = 9.8 \approx 10$  Yes, this matches our expectation.


$V_B$  grounded:  $V_- = -991.02mV, V_{out} = 9.918V, G = \frac{V_{out}}{V_-} = -10$

b) inverting follower

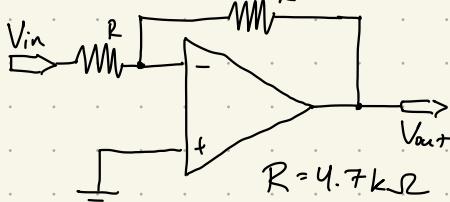


$$V_+ = 477.9mV, V_{out} = 9.66V, V_- = -485.4V$$
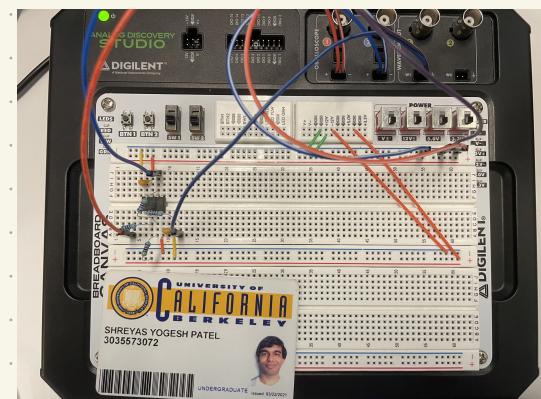
$$V_a = \frac{1}{2}(V_+ - V_-) = 481.65mV, G_a = \frac{V_{out}}{V_a} = 9.99 \approx 10$$



Problem R6.11

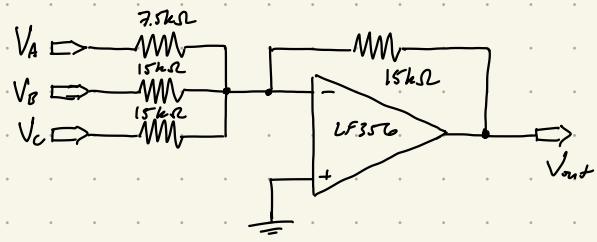

a)  $I = I_A + I_B + I_C$ ,  $I_A = \frac{V_A}{7.5k\Omega}$ ,  $I_B = \frac{V_B}{15k\Omega}$ ,  $I_C = \frac{V_C}{15k\Omega}$

$$I = \frac{2V_A + V_B + V_C}{15k\Omega}$$


$$V_{out} = I R_{fb} = \frac{2V_A + V_B + V_C}{15k\Omega} (15k\Omega) = 2V_A + V_B + V_C$$

b) 

$(V_A, V_B, V_C)$ (v)	expected $V_{out}$ (v)	measured $V_{out}$ (v)
(2.0, -4.0, 3.3)	3.3	3.284
(1.0, -2.0, 5.0)	5.0	4.99

(2.0, -4.0, 3.3)	3.3	3.284
(1.0, -2.0, 5.0)	5.0	4.99

### Problem R6.12

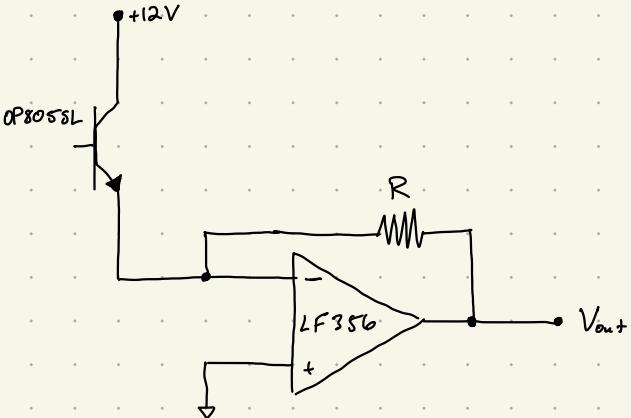

a) start with  $R = 100\text{k}\Omega$

$V_{out}$  is always negative, and is greater magnitude at greater light intensity.

b) Making the room darker decreases the offset.


$$c) f_{3dB} = 91.2 \text{ kHz}$$

$$V_{amp} = 1.3 \text{ V}$$

$$I = \frac{V_{out}}{R} = \frac{1.3 \text{ V}}{100\text{k}\Omega} = 1.3 \text{ mA}$$



### Problem R6.13

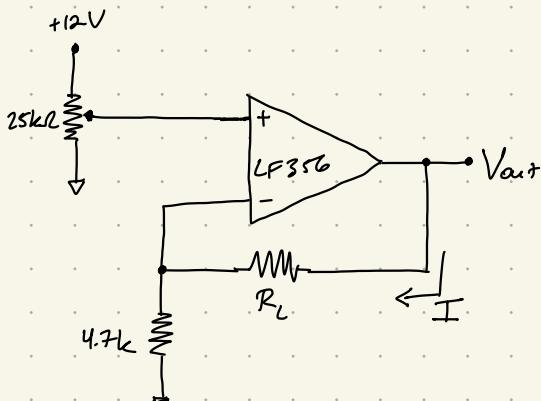

$$R_L = 4.7\text{k}\Omega, I_L = 0.638 \text{ mA}$$

$R_L (\Omega)$	$I_L (\text{mA})$	$V(\text{V})$	$I (\text{mA})$
4.7 k	0.638	1	0.224
47	0.638	3	0.638
47 k	0.203	5	1.058
15 k	0.581		
10 k	0.638		
1	0.638		
0	0.638		

The current decreases when voltage decreases.

The circuit is a constant current source since the op amp wants the  $\Delta V$  between  $V_+$  and  $V_-$  to be 0, so the potential drop across 4.7 kΩ resistor, and therefore current has to be constant. It does this by increasing  $V_{out}$  so the  $\Delta V$  across  $R_L$  rises linearly with  $R_L$  so  $I$  is constant.

Output current is determined by  $V_+$ .  $R_L$  is limited by how high of a  $V_{out}$  the op amp can supply.